


EEL-4713 Computer Architecture Designing a Multiple-Cycle Processor

Outline of today's lecture

- Recap and Introduction
- Introduction to the Concept of Multiple Cycle Processor
- Multiple Cycle Implementation of R-type Instructions
- What is a Multiple Cycle Delay Path and Why is it Bad?
- Multiple Cycle Implementation of Or Immediate
- Multiple Cycle Implementation of Load and Store
- Putting it all Together

1 EEL-4713 Ann Gordon - Ross

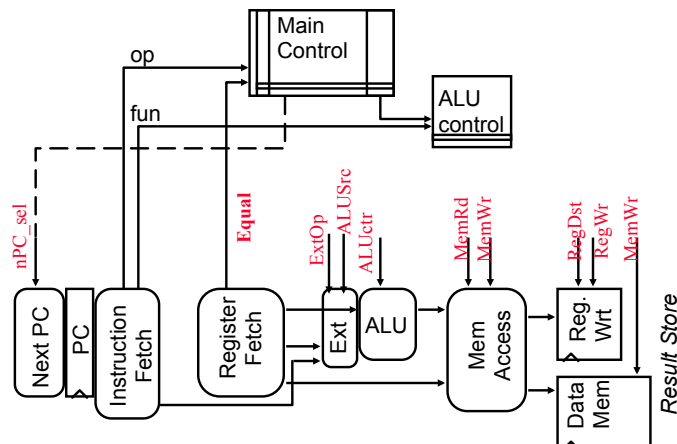Abstract view of our single cycle processor




- looks like an FSM with PC as state


3 EEL-4713 Ann Gordon - Ross

What's wrong with our CPI=1 processor?

Arithmetic & Logical

 

Load

 

Store



Branch



- Long Cycle Time
- All instructions take as much time as the slowest
- Real memory is not so nice as our idealized memory
 - cannot always get the job done in one (short) cycle

4 EEL-4713 Ann Gordon - Ross

Drawbacks of this single cycle processor

- ° Long cycle time:
 - Cycle time is much longer than needed for all other instructions. Examples:
 - R-type instructions do not require data memory access
 - Jump does not require ALU operation nor data memory access
- ° Need for multiple functional units
 - Can't share functional units for multiple operations in the same instruction
 - E.g., instruction/data memory, adders (PC, ALU, branch target, etc.)

5 EEL-4713 Ann Gordon - Ross

Overview of a multiple cycle implementation

- ° The root of the single cycle processor's problems:
 - The cycle time has to be long enough for the slowest instruction
- ° Solution:
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - Cycle time: time it takes to execute the longest step
 - All the steps have similar length
 - This is the essence of the multiple cycle processor
- ° The advantages of the multiple cycle processor:
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete (for now)
 - Load takes five cycles
 - Jump only takes three cycles
 - Allows a functional unit to be used more than once per instruction


6 EEL-4713 Ann Gordon - Ross

What and when:

- ° When designing multi-cycle implementations, you must think about:
 - **What** to do on each cycle
 - **When** results are ready for next cycle
- ° What to do on each cycle:
 - Always need to fetch instruction
 - Always need to decode instruction (know what to do next)
 - Next need to perform actual operation (varies from instruction to instruction)
 - E.g.:
 - Load will require address calculation, memory read, reg write
 - Branch will require comparison and PC update
 - R-type will require ALU operation, reg write


7 EEL-4713 Ann Gordon - Ross

Overview: Control State Diagram

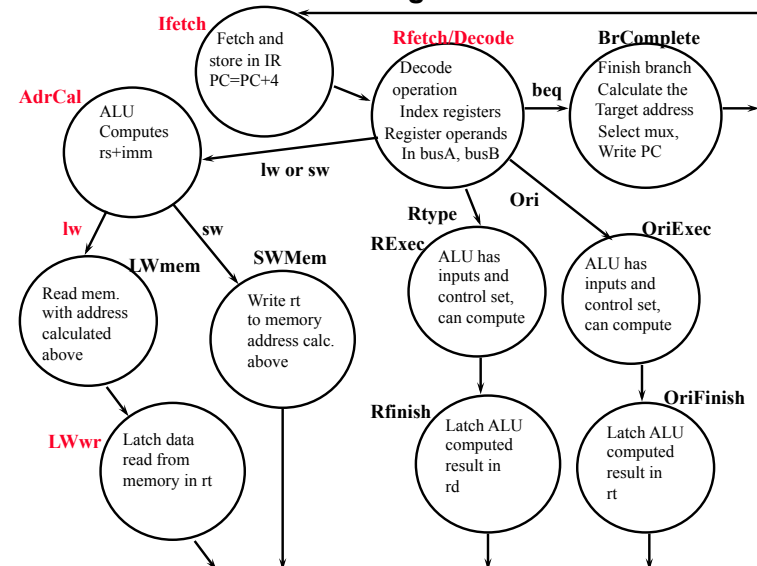

8 EEL-4713 Ann Gordon - Ross

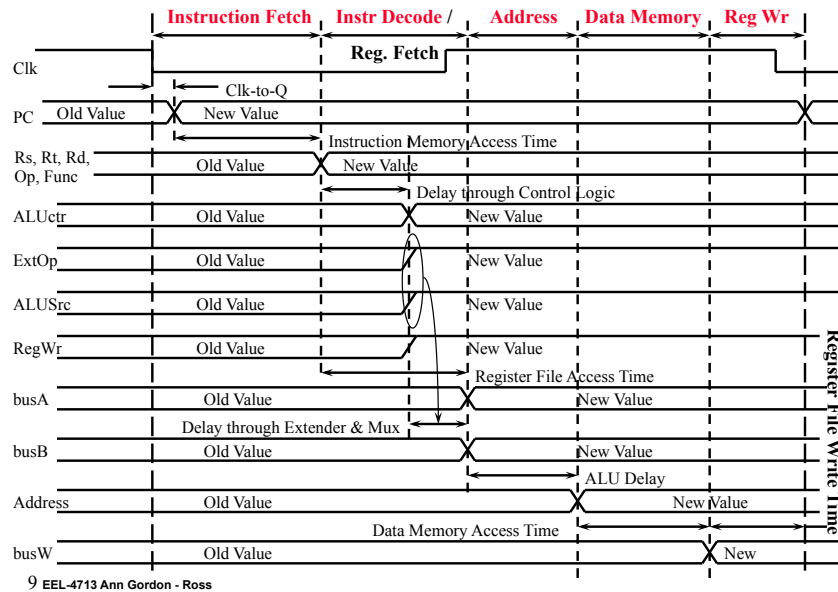
Example: the five steps of a Load instruction




Multicycle datapath

- Similar to the single-cycle datapath; use latches for instruction and branch target address

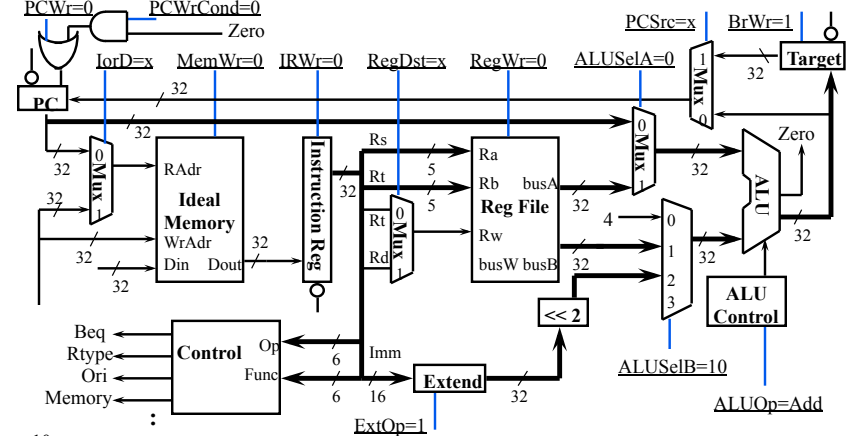
- **Control signals generated for multiple clock cycles per instruction - FSM**



Overview: Control State Diagram

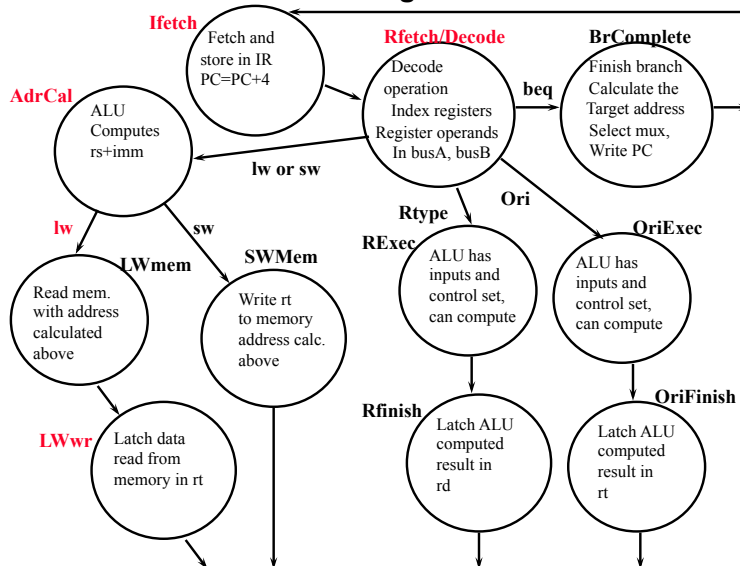


Cycle 1: Fetch

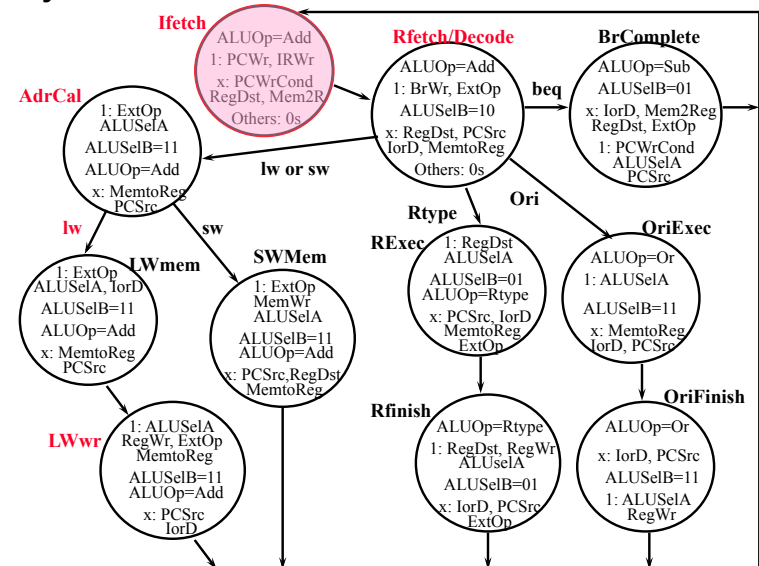

1 Instruction fetch cycle: beginning

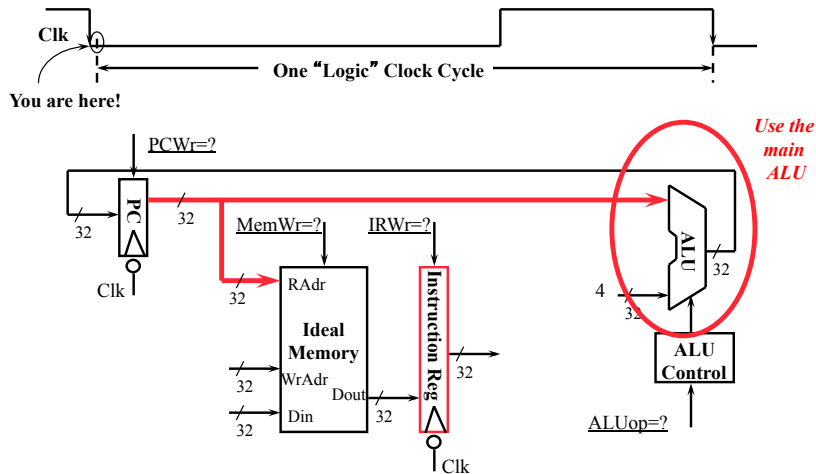
- Every cycle begins right AFTER the clock tick:
 - mem[PC] PC<31:0> + 4



13 EEL-4713 Ann Gordon - Ross

1 Instruction fetch cycle: end

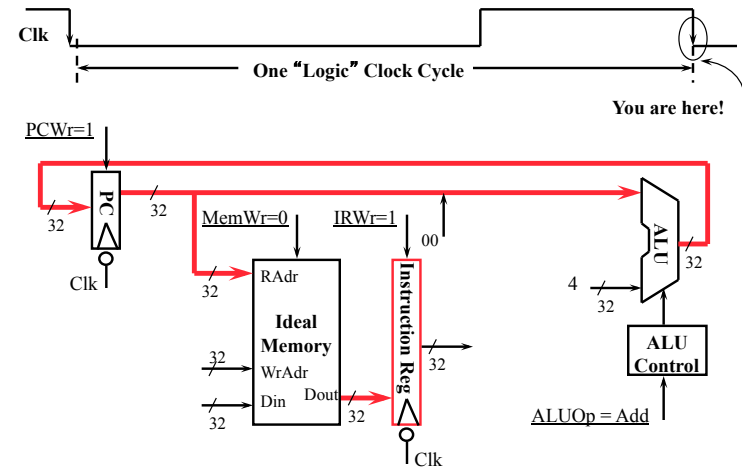
- Every cycle ends AT the next clock tick (storage element updates):
 - $IR \leftarrow mem[PC]$ $PC[31:0] \leftarrow PC[31:0] + 4$



14 EEL-4713 Ann Gordon - Ross


1 Instruction Fetch Cycle: Overall Picture

1. Latch IR=mem[PC]
2. Set PC=PC+4

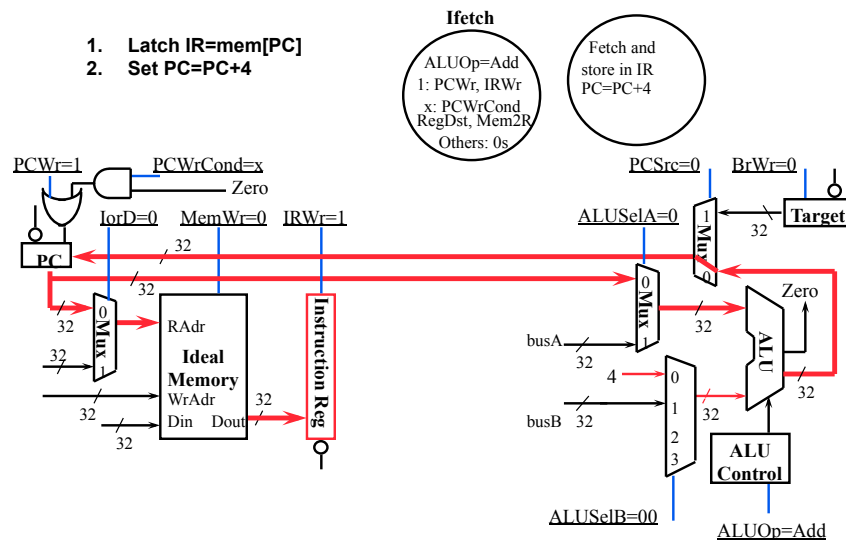

15 EEL-4713 Ann Gordon - Ross


Cycle 2: Register fetch, decode

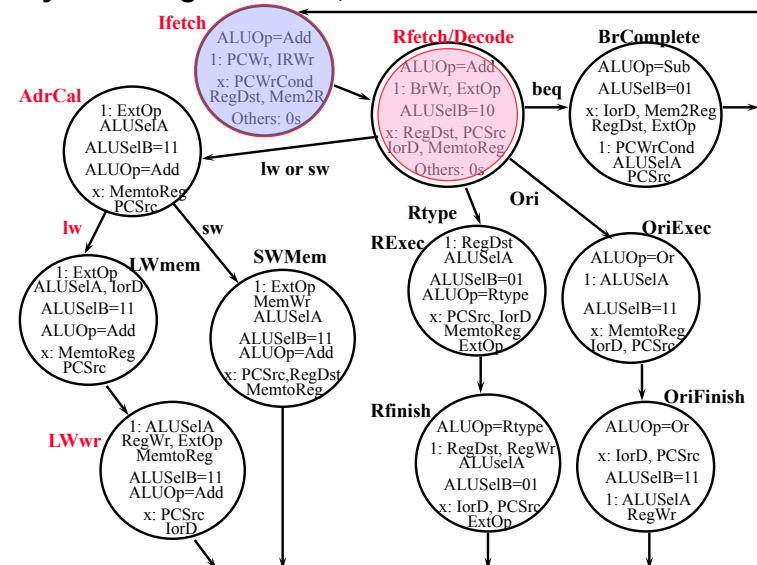

16 EEL-4713 Ann Gordon - Ross

2 Register Fetch / Instruction Decode

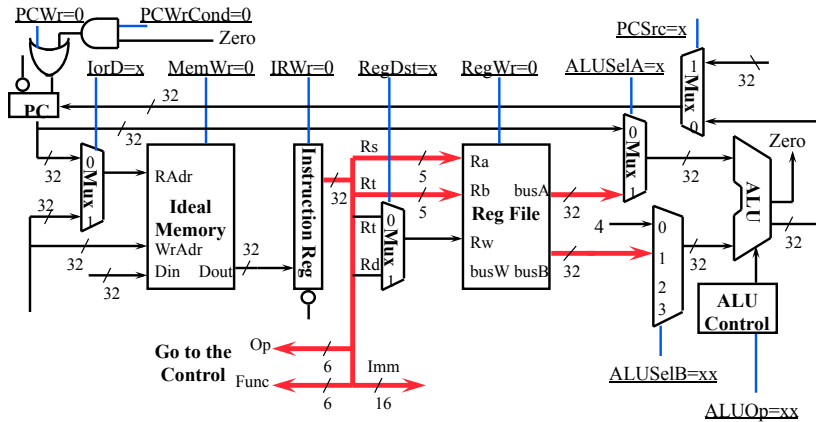
- ° busA <- RegFile[rs] ; busB <- RegFile[rt] ;
- ° ALU can be also be used to compute branch target address (next slide in this cycle (latch target); register compare done on next cycle



17 EEL-4713 Ann Gordon - Ross


2 Register Fetch / Instruction Decode (Continue)

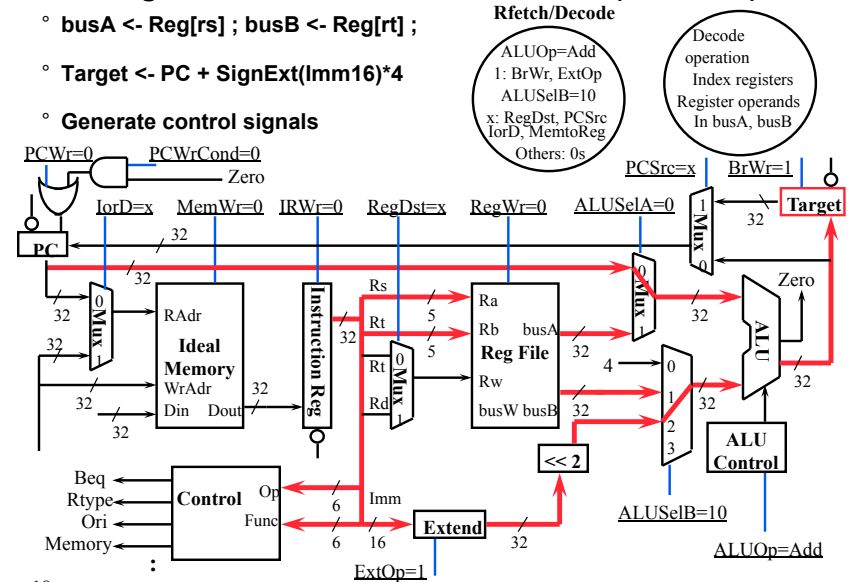- ° busA <- Reg[rs] ; busB <- Reg[rt] ;
- ° Target <- PC + SignExt(Imm16)*4
- ° Generate control signals



18 EEL-4713 Ann Gordon - Ross


Cycle 3: Branch completion

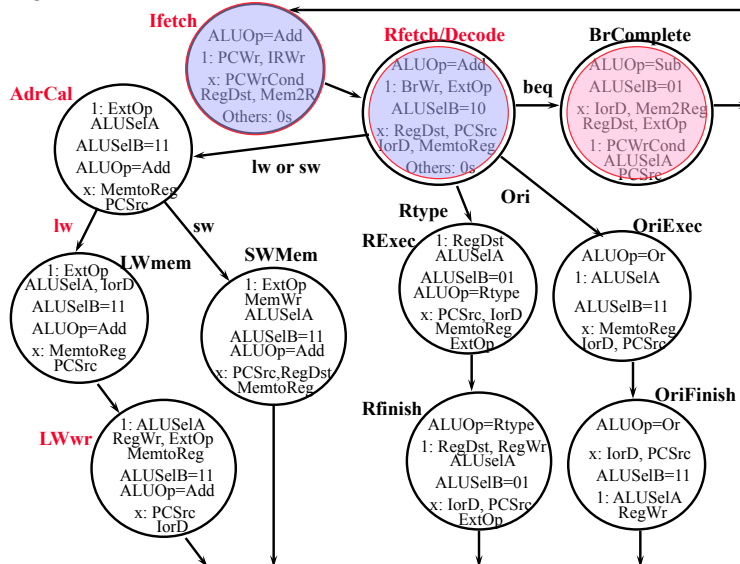

19 EEL-4713 Ann Gordon - Ross


3 Branch Completion

- ° if (busA == busB)
- ° PC <- Target

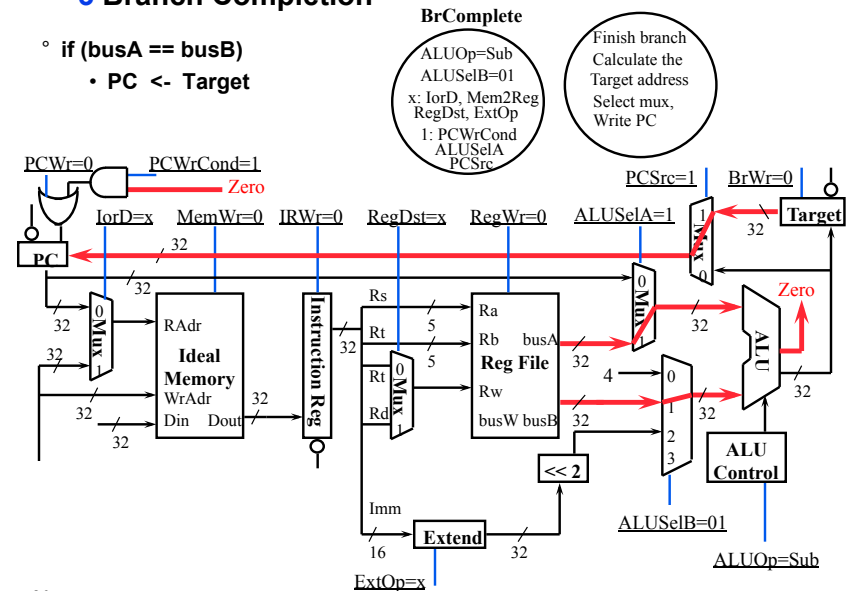


20 EEL-4713 Ann Gordon - Ross

Cycle 3: Rtype execution

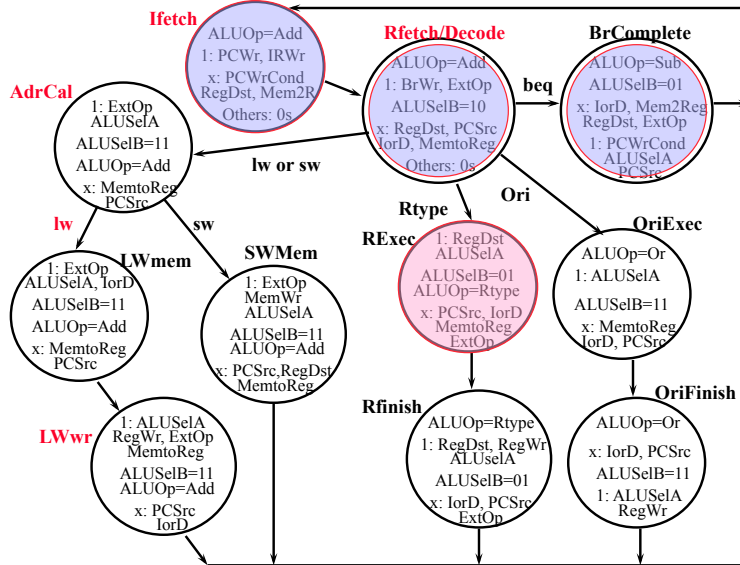

21 EEL-4713 Ann Gordon - Ross


Cycle 4: Rtype completion

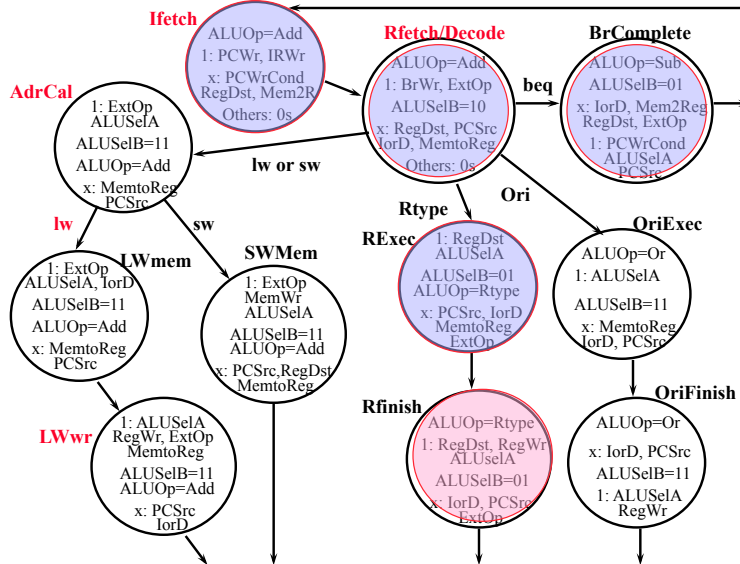

23 EEL-4713 Ann Gordon - Ross

3 R-type Execution


- **ALU Output** <- busA op busB

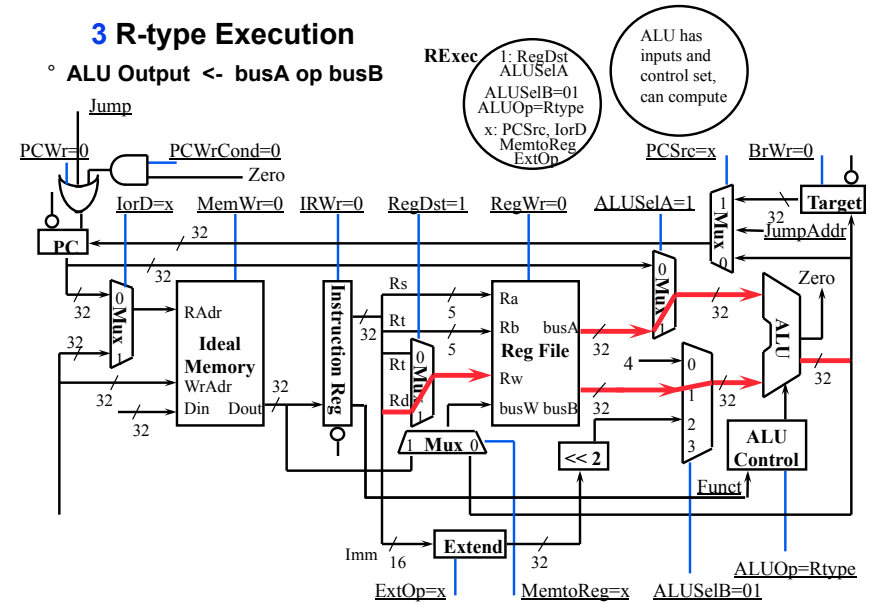

22 EEL-4713 Ann Gordon - Ross


4 R-type Completion

- **R[rd] <- ALU Output**

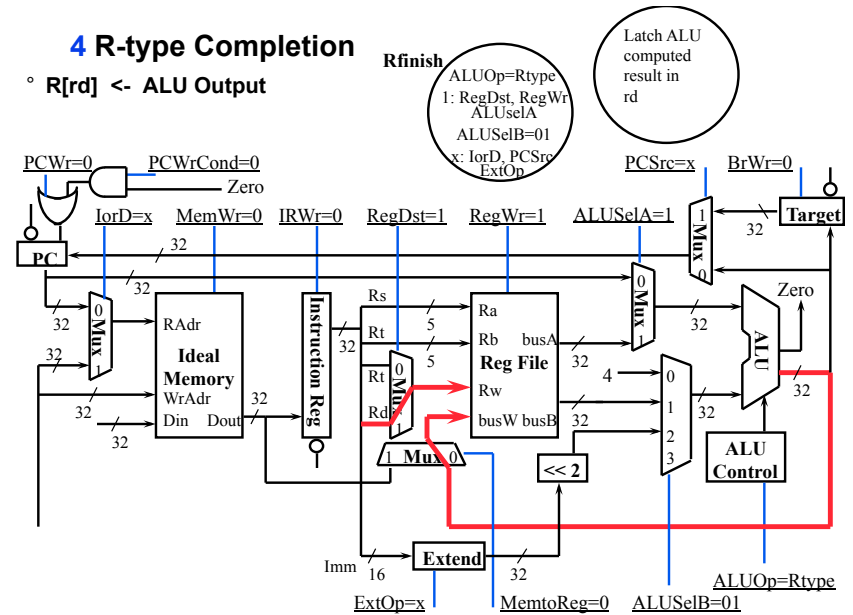


24 EEL-4713 Ann Gordon - Ross

Cycle 3: Ori execution

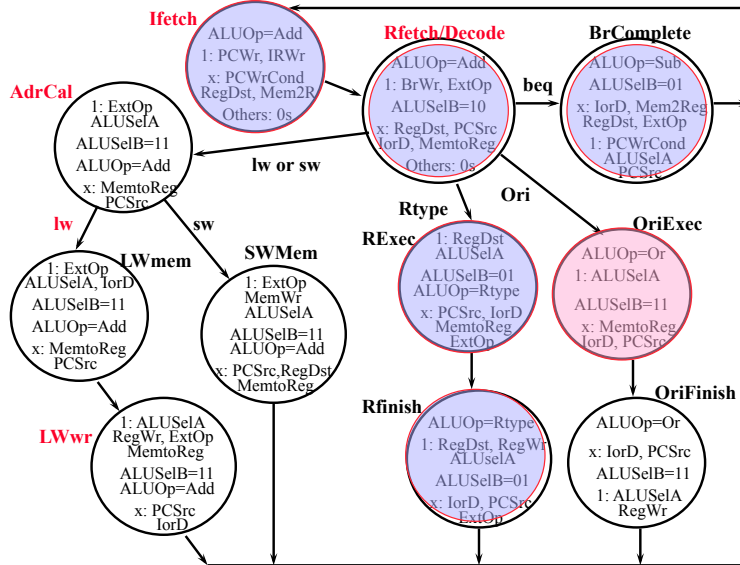

25 EEL-4713 Ann Gordon - Ross


Cycle 4: Ori completion

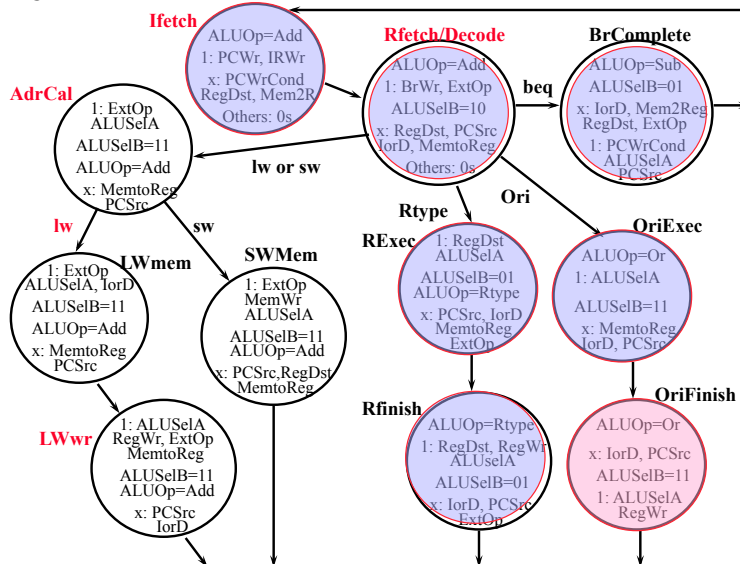

27 EEL-4713 Ann Gordon - Ross

3 Ori Execution

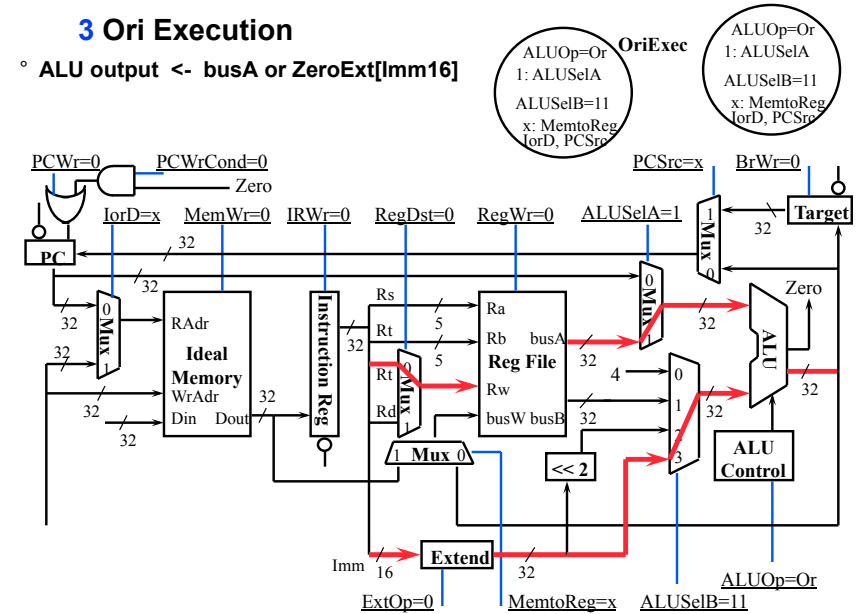
- **ALU output** <- busA or ZeroExt[Imm16]



26 EEL-4713 Ann Gordon - Ross


4 Ori Completion

- **Reg[rt] <- ALU output**

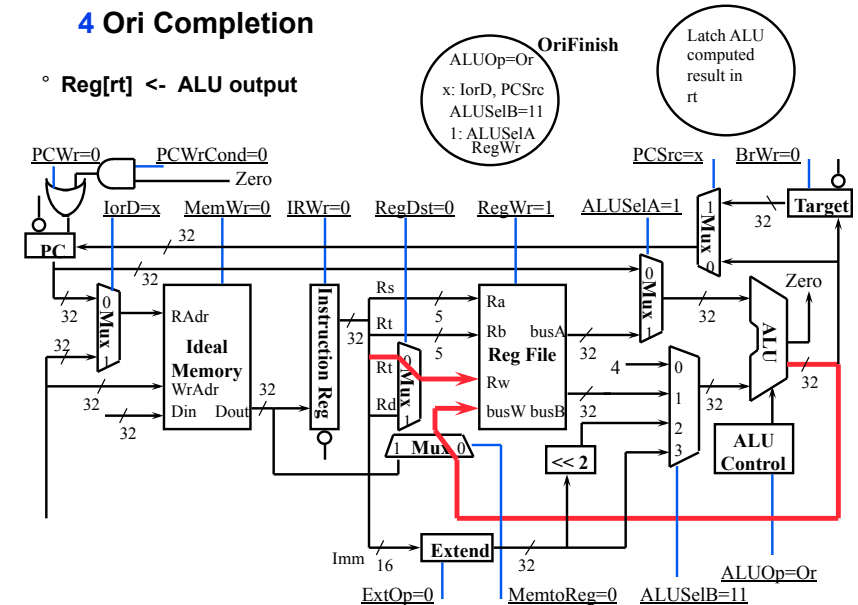


28 EEL-4713 Ann Gordon - Ross

Cycle 3: Address calculation

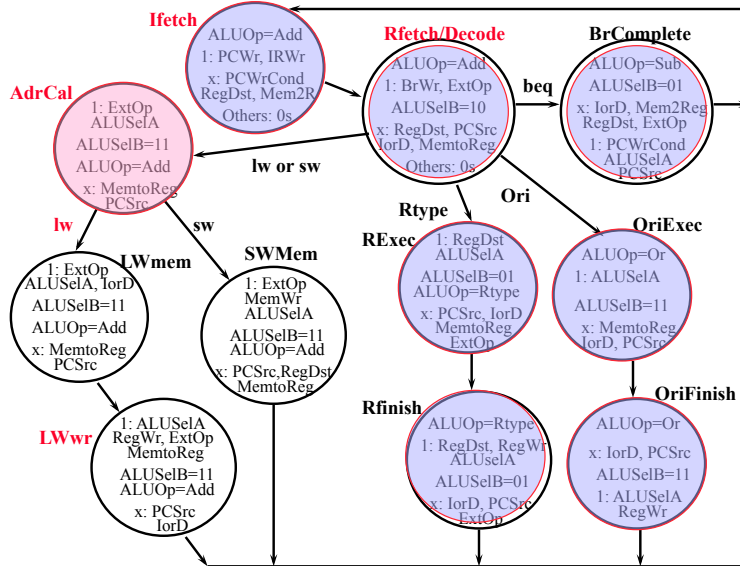


29 EEL-4713 Ann Gordon - Ross

3 Memory Address Calculation

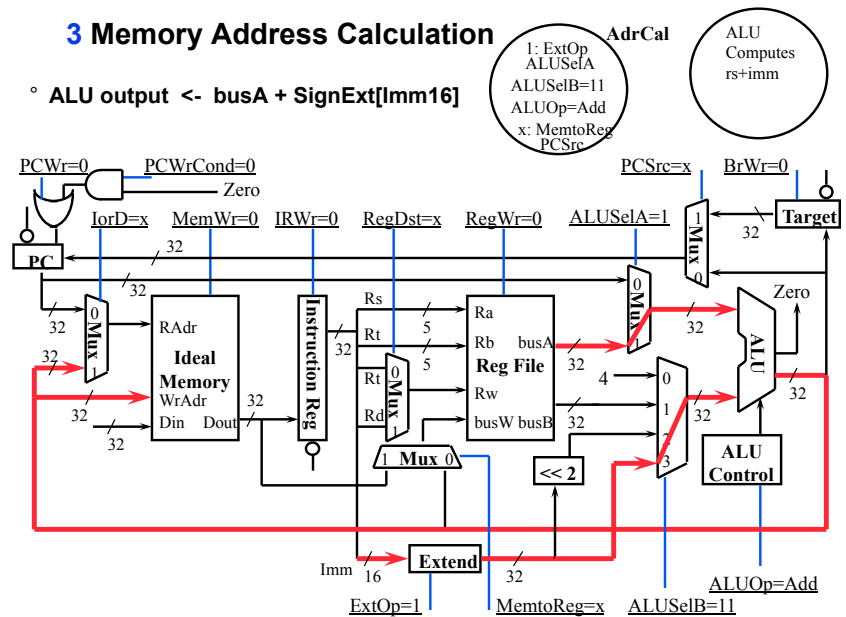


30 EEL-4713 Ann Gordon - Ross

Cycle 4: Memory access, store

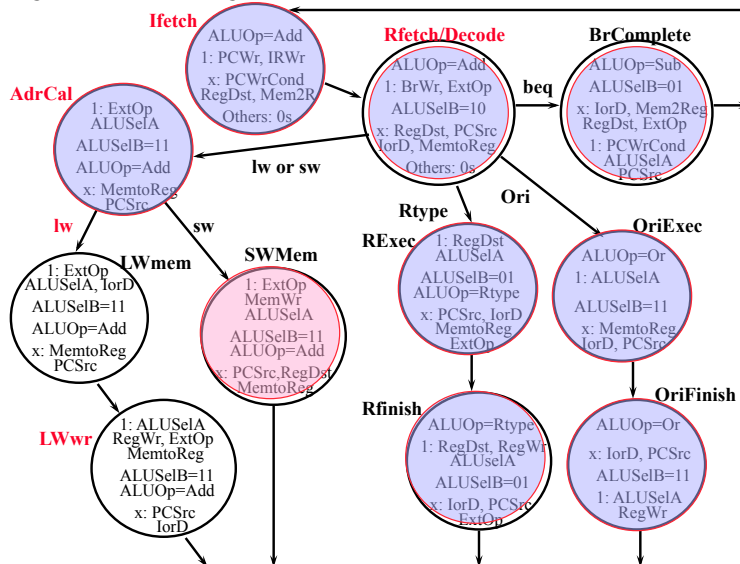


31 EEL-4713 Ann Gordon - Ross

4 Memory Access for Store

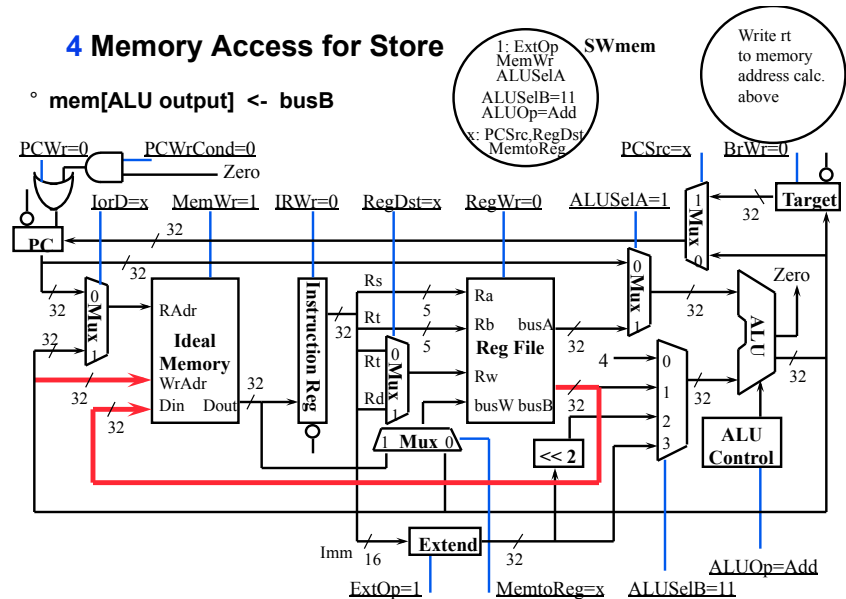

32 EEL-4713 Ann Gordon - Ross


Cycle 4: Memory access, load

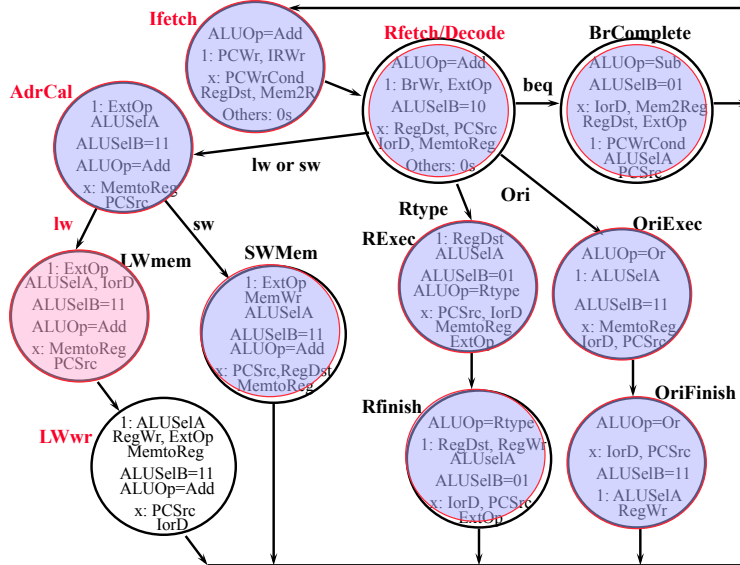

33 EEL-4713 Ann Gordon - Ross


4 Memory Access for Load

◦ Mem Dout <- mem[ALU output]

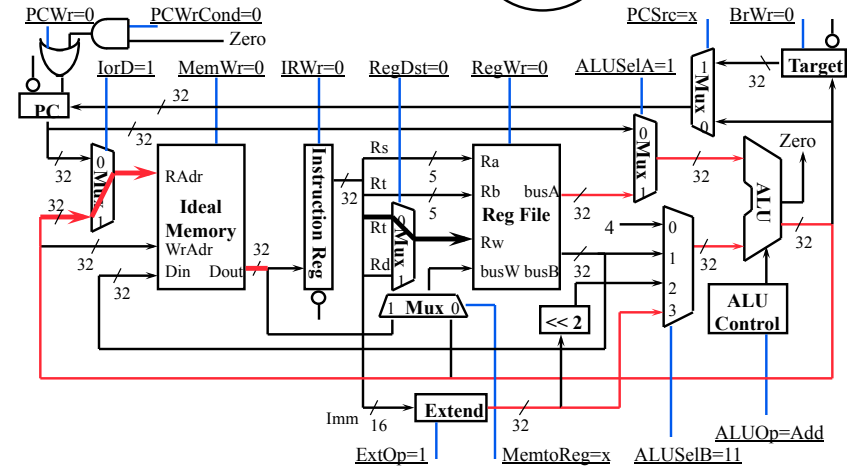

34 EEL-4713 Ann Gordon - Ross


Cycle 4: Memory access, load

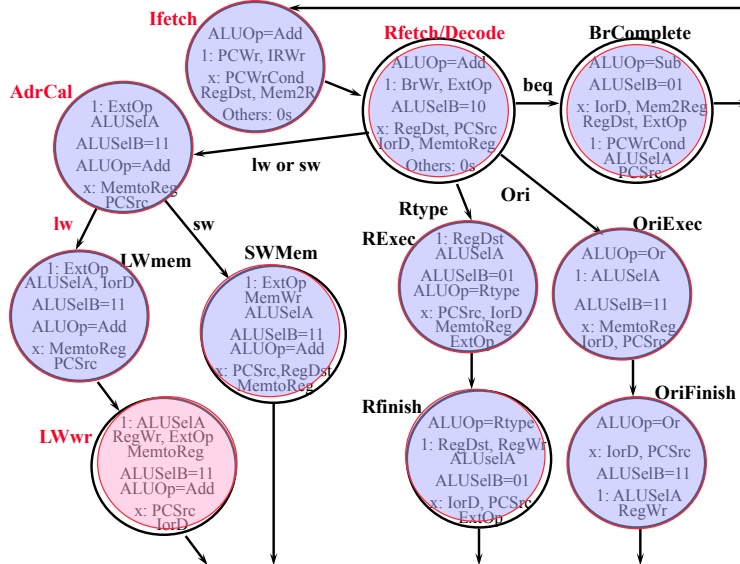

35 EEL-4713 Ann Gordon - Ross


5 Write Back for Load

◦ Reg[rt] <- Mem Dout

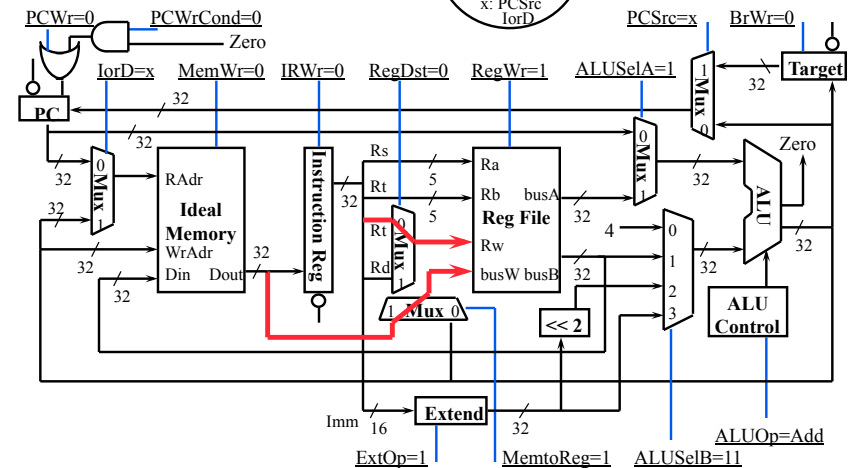


36 EEL-4713 Ann Gordon - Ross

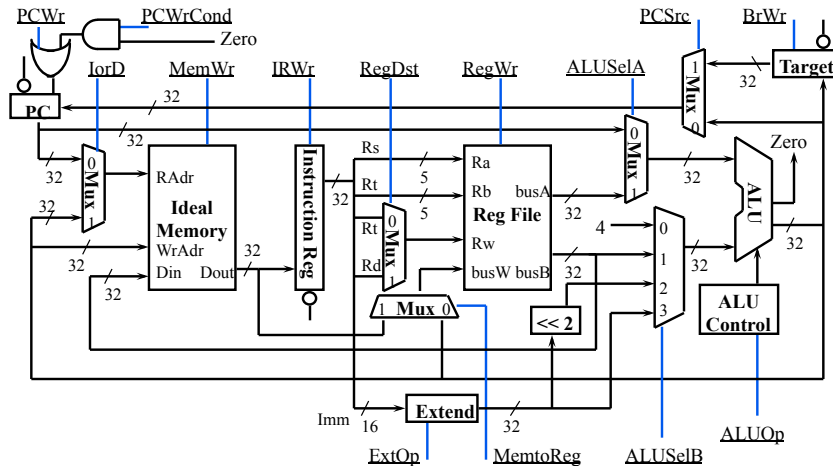Putting it all together: Multiple Cycle Datapath



37 EEL-4713 Ann Gordon - Ross

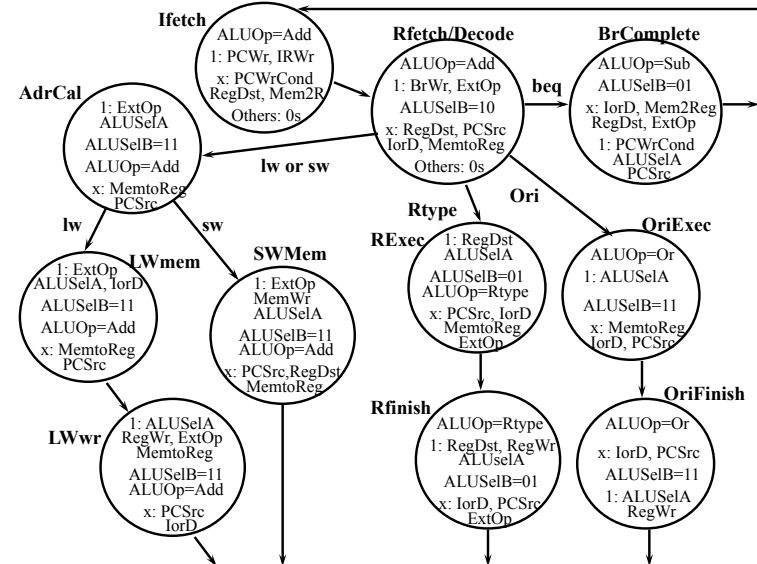
Putting it all together: Control State Diagram



38 EEL-4713 Ann Gordon - Ross

Note: there is a multiple-cycle delay path

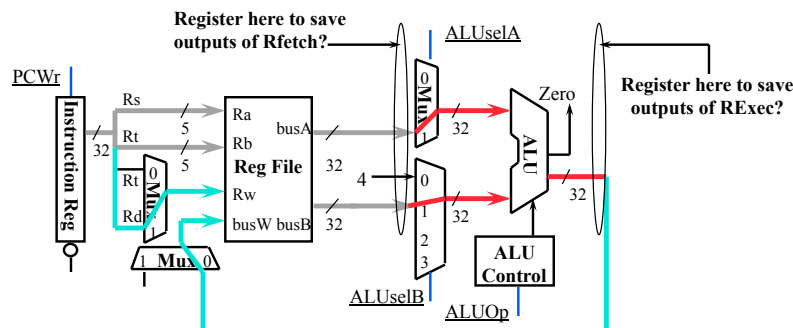- There is no register to save the results between:
 - 2) Register Fetch: $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}]$
 - 3) R-type Execution: $\text{ALU output} \leftarrow \text{busA op busB}$
 - 4) R-type Completion: $\text{Reg}[\text{rd}] \leftarrow \text{ALU output}$



39 EEL-4713 Ann Gordon - Ross


A Multiple Cycle Delay Path (Continue)

- Register is **NOT** needed to save the outputs of Register Fetch:
 - $\text{IRWr} = 0$: busA and busB **will not change** after Register Fetch
- Register is **NOT** needed to save the outputs of R-type Execution:
 - busA and busB **will not change** after Register Fetch
 - Control signals ALUSelA , ALUSelB , and ALUOp **will not change** after R-type Execution
 - Consequently ALU output **will not change** after R-type Execution
- In theory, you need a register to hold a signal value if:
 - (1) The signal is computed in one clock cycle and used in another.
 - (2) **AND** the inputs to the functional block that computes this signal **can change** before the signal is written into a state element.
- You can save a register if Cond 1 is true BUT Cond 2 is false:
 - But in practice, this will introduce a multiple cycle delay path:
 - A logic delay path that takes multiple cycles to propagate from one storage element to the next storage element

40 EEL-4713 Ann Gordon - Ross

Pros and Cons of a Multiple Cycle Delay Path

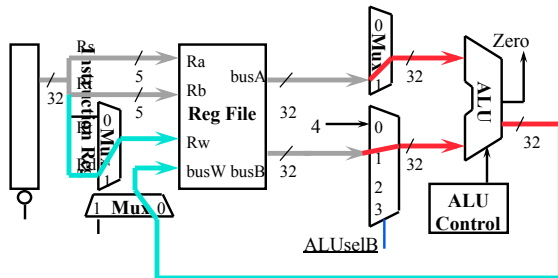- **A 3-cycle path example:**
 - **IR (storage) -> Reg File Read -> ALU -> Reg File Write (storage)**
- **Advantages:**
 - **Register savings**
 - **We can share time among cycles:**
 - **If ALU takes longer than one cycle, still OK as long as the entire path takes less than 3 cycles to finish**



41 EEL-4713 Ann Gordon - Ross


Summary

- Disadvantages of the Single Cycle Processor
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- Multiple Cycle Processor:
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- Do NOT confuse Multiple Cycle Processor with multiple cycle delay path
 - Multiple Cycle Processor executes each instruction in multiple clock cycles
 - Multiple Cycle Delay Path: a combinational logic path between two storage elements that takes more than one clock cycle to complete
- It is possible (desirable) to build a MC Processor without MCDP:
 - Use a register to save a signal's value whenever a signal is generated in one clock cycle and used in another cycle later

43 EEL-4713 Ann Gordon - Ross

Pros and Cons of a Multiple Cycle Delay Path (Continue)

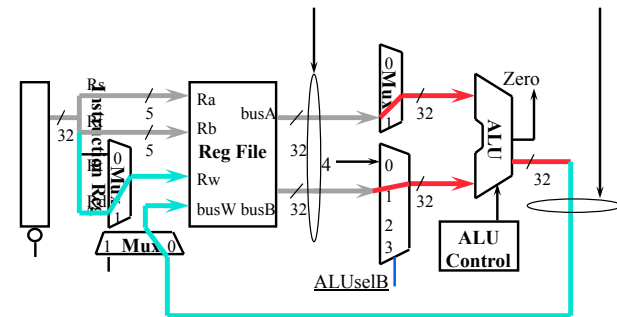- Disadvantage:
 - Static timing analyzer, which ONLY looks at delay between two storage elements, will report this as a timing violation
 - You have to ignore the static timing analyzer's warnings



42 EEL-4713 Ann Gordon - Ross


Control logic

- **Review of Finite State Machine (FSM) control**
- **From Finite State Diagrams to Microprogramming**

44 EEL-4713 Ann Gordon - Ross


Overview

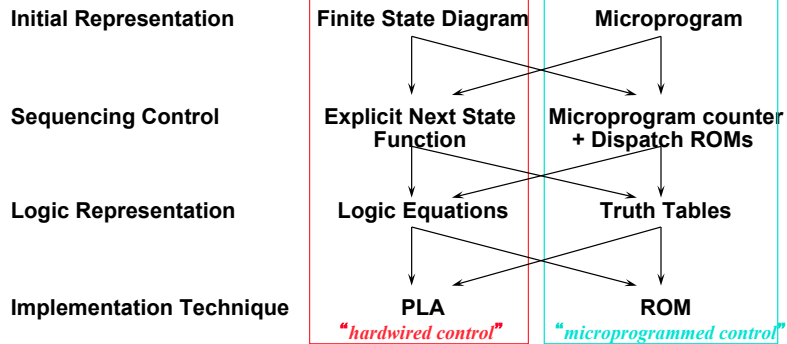- Control may be designed using one of several initial representations. The choice of sequence control, and how logic is represented, can then be determined independently; the control can then be implemented with one of several methods using a structured logic technique.




45 EEL-4713 Ann Gordon - Ross

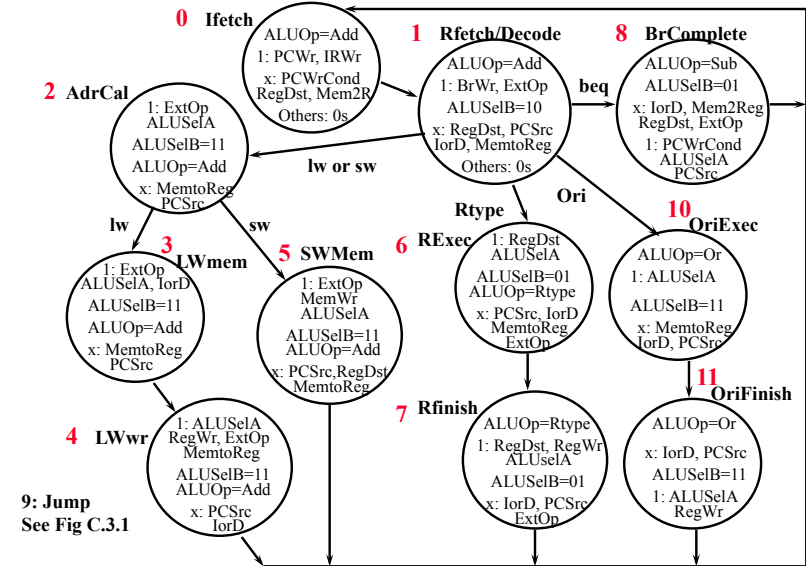Initial Representation: Finite State Diagram



46 EEL-4713 Ann Gordon - Ross

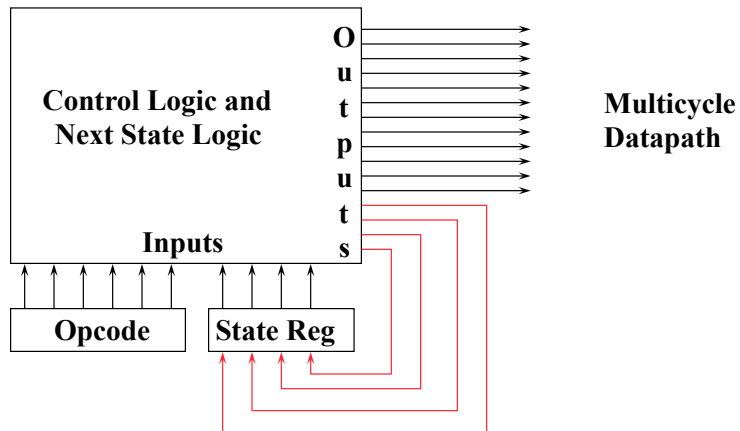
Sequencing Control: Explicit Next State Function



- Next state number is encoded just like datapath controls

47 EEL-4713 Ann Gordon - Ross

Interface in detail

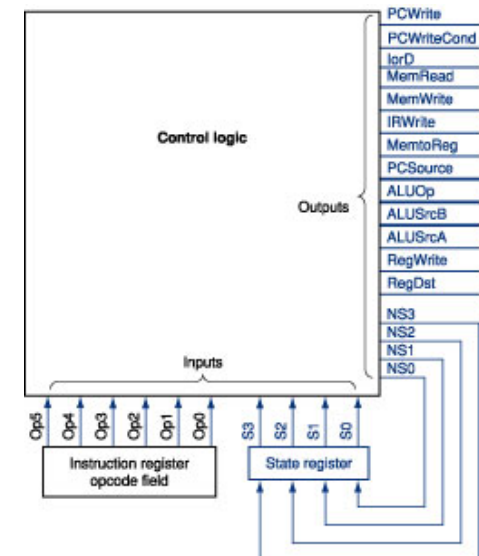

48 EEL-4713 Ann Gordon - Ross

Logic Representation: Logic Equations

° Next state from current state

- State 0 -> State 1
- State 1 -> S2, S6, S8, S10
- State 2 -> S3, S5
- State 3 -> State 4
- State 4 -> State 0
- State 5 -> State 0
- State 6 -> State 7
- State 7 -> State 0
- State 8 -> State 0
- State 9 -> State 0
- State 10 -> State 11
- State 11 -> State 0


° Alternatively, prior state & condition

- S4, S5, S7, S8, S9, S11 -> State 0
- State 0 _____ -> State 1
- State 1 & op = lw/sw -> State 2
- State 2 & op = lw _____ -> State 3
- State 3 _____ -> State 4
- State 2 & op = sw _____ -> State 5
- State 1 & op = R-type -> State 6
- State 6 _____ -> State 7
- State 1 & op = beq _____ -> State 8
- State 2 & op = jmp _____ -> State 9
- State 1 & op = ORi _____ -> State 10
- State 10 _____ -> State 11

See Fig. C.3.3


Implementation Technique: Programmed Logic Arrays

 - ° Each output line: the logical OR of logical AND of input lines or their complement; AND minterms specified in top AND plane, OR sums specified in bottom OR plane



Implementation Technique: Programmed Logic Arrays

 - ° Each output line the logical OR of logical AND of input lines or their complement; AND minterms specified in top AND plane, OR sums specified in bottom OR plane




Multicycle Control

- ° Given numbers assigned to FSM, can in turn determine next state as function of the inputs and current state
- ° Can turn these into Boolean equations for each bit of the next state lines
 - Implement easily using PLA (programmable logic array) or ROM storing truth tables
 - See Figs. C.3.6 and C.3.8 for tables showing outputs and next state as function of current state and opcode
- ° What if many more states, many more conditions?
 - State machine gets too large; very large ROMs/PLAs
- ° What if need to add a state?
 - May need to increase address for ROM, number of inputs for PLA gates
- ° Or just implement FSM in VHDL


Next Iteration: Using Sequencer for Next State

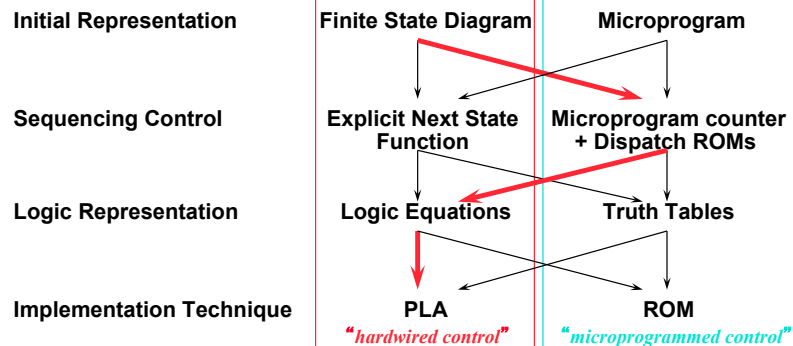- Before: Explicit Next State; Next try variation 1 step from right hand side
- Few sequential states in small FSM: suppose added floating point?
- Still need to go to non-sequential states: e.g., state 1 => 2, 6, 8, 10



53 EEL-4713 Ann Gordon - Ross

Sequencer-based control unit

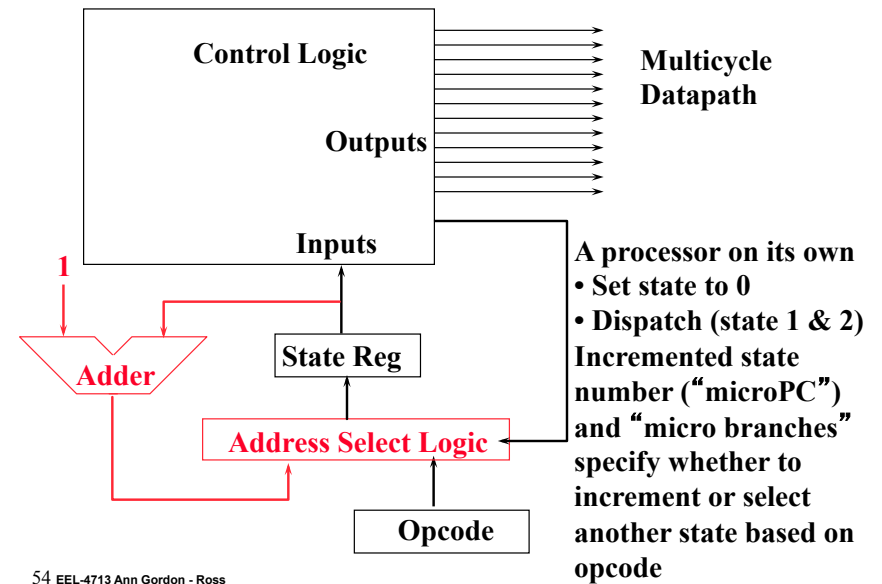

54 EEL-4713 Ann Gordon - Ross

Sequencer-based control unit

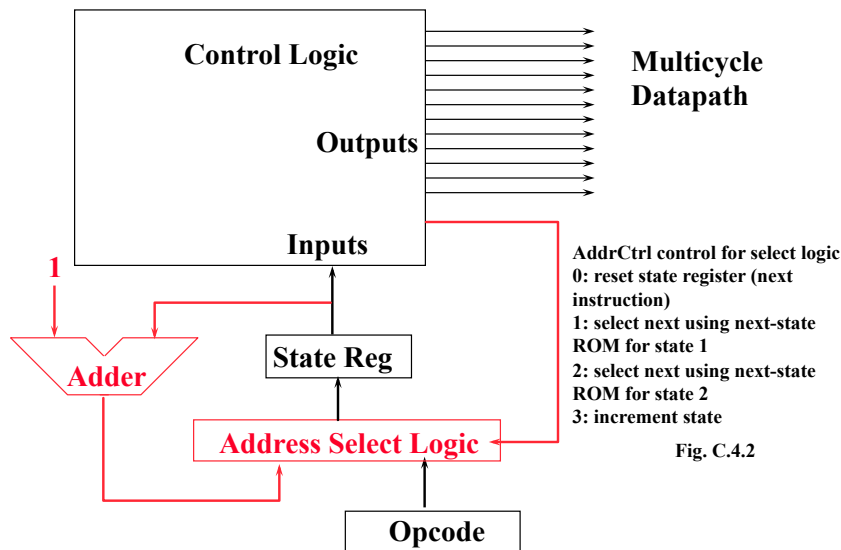



Fig. C.4.2

55 EEL-4713 Ann Gordon - Ross

Sequencer block diagram

Before: 6bit opcode + 4-bit state -> 4-bit NS

Now: 4-bit state -> 2-bit AddrCtrl

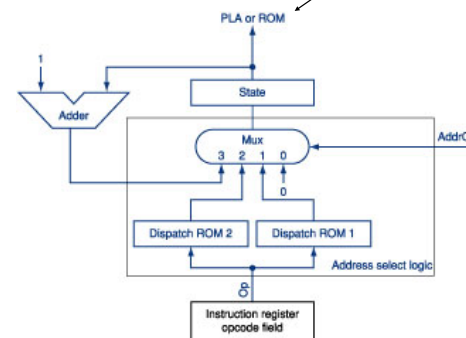


0000 – AddrCtrl=3 (fetch)
0001 – AddrCtrl=1 (decode)
0010 – AddrCtrl=2 (lw/sw)
0011 – AddrCtrl=3 (lw)
0100 – AddrCtrl=0 (lw)
0101 – AddrCtrl=0 (sw)
0110 – AddrCtrl=3 (r-type)
0111 – AddrCtrl=0 (r-type)
1000 – AddrCtrl=0 (branch)
1010 – AddrCtrl=3 (ori)
1011 – AddrCtrl=0 (ori)

Dispatch ROM 1 (Indexed by opcode)
lw -> 0010
sw -> 0010
R-type -> 0110
ori -> 1010
branch -> 1000

ROM2:
lw -> 0011
sw -> 0101


56 EEL-4713 Ann Gordon - Ross

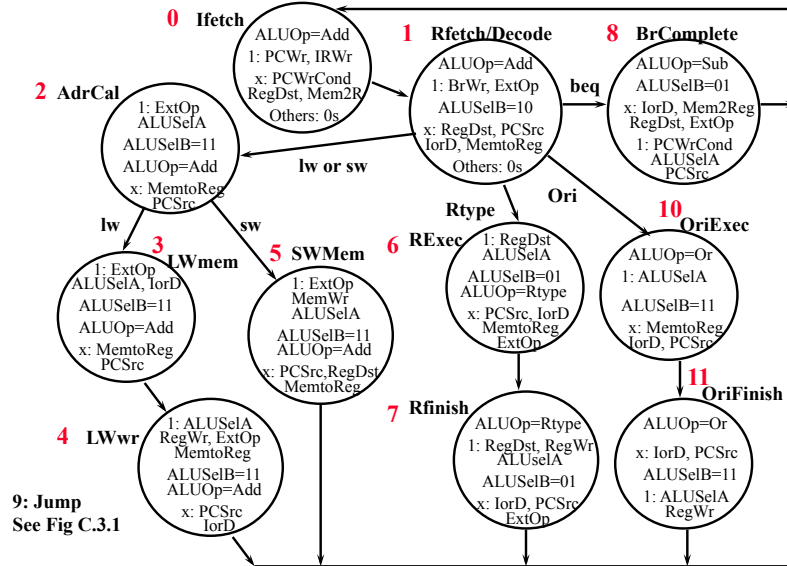Initial Representation: Finite State Diagram



57 EEL-4713 Ann Gordon - Ross

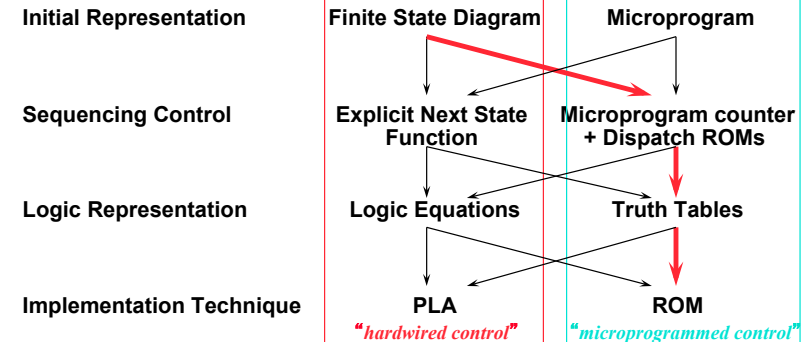Next Iteration: Using Microprogram for Representation



- ROM can be thought of as a sequence of control words
- Control word can be thought of as instruction: "microinstruction"

58 EEL-4713 Ann Gordon - Ross

Microprogramming

- Control is the hard part of processor design
 - Datapath is fairly regular and well-organized
 - Memory is highly regular
 - Control is irregular and global

Microprogramming:


- A particular strategy for implementing the control unit of a processor by "programming" at the level of register transfer operations

Microarchitecture:

- Logical structure and functional capabilities of the hardware as seen by the microprogrammer

59 EEL-4713 Ann Gordon - Ross

Macroinstruction Interpretation

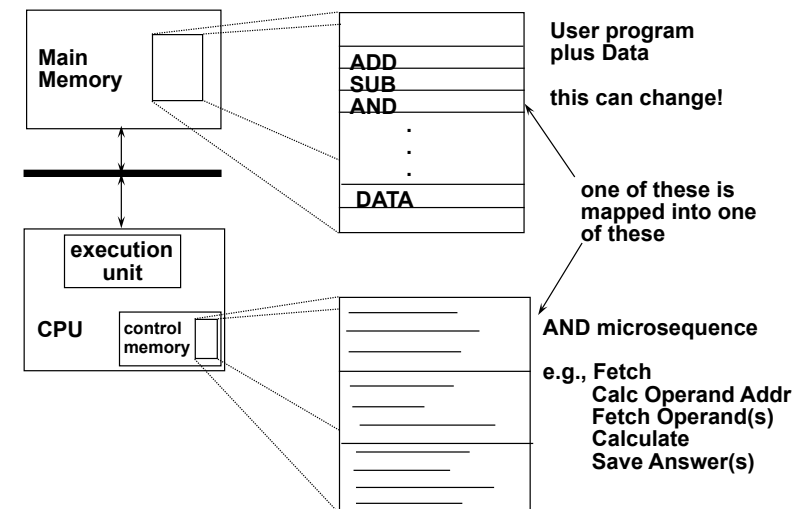

60 EEL-4713 Ann Gordon - Ross

Microprogramming Pros and Cons

- Ease of design
- Flexibility
 - Easy to adapt to changes in organization, timing, technology
 - Can make changes late in design cycle, or even in the field
- Can implement very powerful instruction sets (just more control memory)
- Generality
 - Can implement multiple instruction sets on same machine.
 - Can tailor instruction set to application.
- Compatibility
 - Many organizations, same instruction set
- Costly to implement
- Slow

Summary: Multicycle Control

- Microprogramming and hardwired control have many similarities, perhaps biggest difference is initial representation and ease of change of implementation, with ROM generally being easier than PLA

