

Assignment #2

EEL4713

Peter Borenstein

January 28<sup>th</sup>, 2012

## Introduction

This assignment focused on propagation delays of two basic devices, multiplexers and D-flipflops. The registers used in this course are 32 bits wide. Various sized muxes were made leading up to a 32 bit 2:1 mux. A component was built that zero or sign extends a 16 bit number to a 32 bit number. It is important to pay attention to propagation to set the right clock speed. If a clock were to trigger in the middle of propagation, the device would be processing garbage data.

## Design and testing

The multiplexers were built first. The 2:1 multiplexer has two inputs, in0 and in1, and the select input, sel, chooses which input is seen at the output. The inputs used were 1, 5 and 32 bits wide. There were only two inputs, so the select signal was only one bit.

	1 bit mux	5 bit mux	32 bit mux
Worst delay	11.7ns	13.6ns	18.5ns

Q 3.2: Rs, Rt, and Rd are represented by 5 bit numbers because there are 32 registers. 5 bits can make 32 combinations, or one for every register.

Q 3.5: The propagation increased as the size of the mux increased. This indicates that the chip being used can't simply arrange muxes in parallel.

The 32 bit register was created next. The register has an input, D, and an output Q. Q acquires and holds the value of D if the write bit is true during a rising clock edge. The clock edge could be falling if the designer chose it to be so. There is an asynchronous clear that sets the values of Q to zero. The delay for Q to acquire the value D is 13 ns.

Q 3.5: The clock period must be greater than the largest propagation delay. For the register to work properly, the clock cannot be faster than 77MHz.

The extender was built last. Immediate instructions only have 16 bits to work with due to limited instruction length. A 32 bit number is needed to perform arithmetic functions with 32 bit numbers. This device compensates for that by filling in the upper 16 bits with 0's or 1's for negative numbers. A zero extender was built that takes in a 16 bit number and outputs a 32 bit number with its upper 16 bits set to 0. Then a sign extender was built to fill in the upper 16 bits of the output with 1's. These devices are combined and a one bit select signal is created to choose between the two.

### **Textbook questions**

2.11.4 a) R-type

b) I-type

2.11.5 a) add

b) sw

2.11.6 a) 00000000000100010000110000010000

b) 101011100000101000000000000010

## Appendix

### Mux code:

```
library ieee;
use ieee.std_logic_1164.all;
entity mux1 is
port ( sel : in std_logic;
      in1, in0 : in std_logic_vector(31 downto 0); --31 can be changed for the 5 and 1 bit muxes
      output : out std_logic_vector(31 downto 0)
    );
end mux1;
architecture behavior of mux1 is
begin
    with sel select
        output<=      in1 when '1',          --with select select lol
                     in0 when others;        -- output= sel and in1 or not sel and in0
end behavior;
```

### Register code:

```
library ieee;
use ieee.std_logic_1164.all;
entity reg32 is
port ( D          : in std_logic_vector(31 downto 0);
      clk, clr, wr : in std_logic;
      Q          : out std_logic_vector(31 downto 0)
    );
end reg32;
architecture behavior of reg32 is
begin
    process(clk, clr)
    begin
        if clr='1' then          --clr sets Q to 0 asynchronously
            Q<=(others=>'0');
        elsif(clk'event and clk='1' and wr='1') then -- conditions for Q to obtain a value
            Q<=D;
        end if;
    end process;
```

Zeroext, Signext, and Extender code:

library ieee;

use ieee.std\_logic\_1164.all;

entity extender is

port ( in0 : in std\_logic\_vector(15 downto 0); --input is 16 bits

sel : in std\_logic;

out0 : out std\_logic\_vector(31 downto 0) --output is 32 bits

);

end extender;

architecture behavior of extender is

begin

with sel select

out0 <= x"ffff"&in0 when '1',

x"0000"&in0 when others;

end behavior;

architecture behavior of zeroext is

begin

out0 <= x"0000"&in0; --concatenate with 0's


end behavior;

architecture behavior of signext is


begin

out0 <= x"ffff"&in0 --concatenate with 1's

end behavior;

 


 The extender fills the upper 16 bits with 1s or 0s determined by sel. On the left half of the waveform, sel is 0 so the upper bits are filled with 0. On the right, sel=1 and the upper bits of out0 are all 1. the delay is 9.7ns




vector is not important. I used it to simulate all the input values.

 
At the cursor we see that the output changed at 161.2 ns. this is because in1 changed at 100 ns. Our delay is 11.2 ns.



 
Here we have a 5 bit 2:1 mux. The select is changed. The output changes from in1 to in2. The output changes 13.2ns after the select bit switched due to propagation delay.



 
The is the waveform of a 32 bit 2:1 mux. A select change is shown. The output changes to in0 16.7ns after the select bit changes.



 The sign extender sets the upper 16 bits of the output to 1. the cursor points out a 10.5 ns delay. the redix is hexadecimal



 Here we have a zero extension. The inputs are 7FFF and FFFF. We see the upper 16 bits of the output are set to zero after a 10.5ns delay.



This is a 32 bit register. It is set to 0x00000000 initially, then to 0x1234abcd, and then to 0xABCD1234. The clk period is 40 ns. The propagation delay is about 13ns as seen at the cursor (the clock triggered the change at 20 ns).