

EEL-4713C Computer Architecture Designing a Pipelined Processor

Outline

- Introduction to the pipelined datapath/control
 - Key concepts and examples
 - Beginning with multi-cycle datapath
- Reading:
 - 4.5-4.9

EEL-4713 Ann Gordon-Ross 1

Recap: Multiple Cycle Implementation

- Break the instruction into smaller steps
- Execute each step (instead of the entire instruction) in one cycle
 - Strive to keep steps with similar length
- Instructions take multiple cycles to execute
 - Only one instruction uses the datapath at any given cycle
- Pipelining
 - Goal: improve performance by having *multiple instructions in the datapath at any given cycle*

EEL-4713 Ann Gordon-Ross 3

EEL-4713 Ann Gordon-Ross 2


Pipelining is Natural!

- Laundry Example
- Alice, Bob, Charlie, and Debbie each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Drier takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers




EEL-4713 Ann Gordon-Ross 4

Sequential Laundry

 


EEL-4713 Ann Gordon-Ross 5

Pipelined Laundry: Start work ASAP

 

EEL-4713 Ann Gordon-Ross 6

Pipelining Lessons

 

- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number of pipe stages**
- Also:
 - Pipeline rate limited by **slowest** pipeline stage
 - Unbalanced lengths of pipe stages reduces speedup
 - Time to "**fill**" pipeline and time to "**drain**" it reduces speedup
 - Dependences - stalls

EEL-4713 Ann Gordon-Ross 7

Why Pipeline?

- Suppose we execute 100 instructions
- Single Cycle Machine, 220MHz
 - $4.5 \text{ ns/cycle} \times 1 \text{ CPI} \times 100 \text{ inst} = 450 \text{ ns}$
- Multicycle Machine, 1GHz, average CPI 4.6
 - $1 \text{ ns/cycle} \times 4.6 \text{ CPI} \times 100 \text{ inst} = 460 \text{ ns}$
- Ideal pipelined machine, 1GHz
 - $1 \text{ ns/cycle} \times (1 \text{ CPI} \times 100 \text{ inst} + 4 \text{ cycle drain}) = 104 \text{ ns}$

EEL-4713 Ann Gordon-Ross 8


Datapath: from multicycle to pipelined

Key approach:

- Begin by considering each cycle a pipeline stage
- Add registers between consecutive stages to store data and control bits flowing from one stage to the next
- Add logic to deal with “hazards”
 - Ensure functional units are not used by more than one stage at the same time
 - Ensure producer/consumer dependences are not violated


Example: load instruction

Timing Diagram of a Load Instruction

 


EEL-4713 Ann Gordon-Ross 9

The Five Stages of Load

 

- Ifetch: Instruction Fetch
 - Fetch the instruction from the Instruction Memory
- Reg/Dec: Registers Fetch and Instruction Decode
- Exec: Calculate the memory address
- Mem: Read the data from the Data Memory
- Wr: Write the data back to the register file

Pipelining the Load Instruction

 


- The five independent functional units in the pipeline datapath are:
 - Instruction Memory for the Ifetch stage
 - Register file: read ports (bus A and busB) for the Reg/Dec stage
 - ALU for the Exec stage
 - Data Memory for the Mem stage
 - Register File's Write port (bus W) for the Wr stage
- One instruction enters the pipeline every cycle
 - One instruction comes out of the pipeline (complete) every cycle
 - The effective cycles per Instruction (CPI) is 1

EEL-4713 Ann Gordon-Ross 11


EEL-4713 Ann Gordon-Ross 12

 Why Pipeline? Because the resources are there!




EEL-4713 Ann Gordon-Ross 13

 Conventional Pipelined Execution Representation



EEL-4713 Ann Gordon-Ross 14

 Single Cycle, Multiple Cycle, vs. Pipeline




EEL-4713 Ann Gordon-Ross 15

*Can pipelining get us into trouble?


- Yes: **Pipeline Hazards**
 - **structural hazards**: attempt to use the same resource two different ways at the same time
 - E.g., combined washer/dryer would be a structural hazard or folder busy doing something else (watching TV)
 - **data hazards**: attempt to use item before it is ready
 - E.g., one sock of pair in dryer and one in washer; can't fold until get sock from washer through dryer
 - instruction depends on result of prior instruction still in the pipeline
 - **control hazards**: attempt to make a decision before condition is evaluated
 - branch instructions
- Can always resolve hazards by **waiting**
 - pipeline control must detect the hazard
 - take action (or delay action) to resolve hazards

EEL-4713 Ann Gordon-Ross 16

Single Memory is a Structural Hazard

 

The Four Stages of R-type

 


- **Ifetch: Instruction Fetch**
 - **Fetch the instruction from the Instruction Memory**
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU operates on the two register operands**
- **Wr: Write the ALU output back to the register file**

Structural Hazards limit performance

 - **Example: if average 1.3 memory accesses per instruction and only one memory access per cycle then**
 - **average CPI ≥ 1.3**
 - **otherwise resource is more than 100% utilized**
 - **More on Hazards later**

Pipelining the R-type and Load Instruction




- **We have a problem:**
 - **Two instructions try to write to the register file at the same time!**


Important Observation

- Each functional unit can only be used once per instruction
- Each functional unit must be used at the same stage for all instructions:

 - Load uses Register File's Write Port during its 5th stage




 - R-type uses Register File's Write Port during its 4th stage



EEL-4713 Ann Gordon-Ross 21

 Solution 1: Insert "Bubble" into the Pipeline





- Insert a "bubble" into the pipeline to prevent 2 writes at the same cycle
- The control logic can be complex

EEL-4713 Ann Gordon-Ross 22


Solution 2: Delay R-type's Write by One Cycle

  - Delay R-type's register write by one cycle:
 - Now R-type instructions also use Reg File's write port at Stage 5
 - Mem stage is a NOOP stage: nothing is being done



EEL-4713 Ann Gordon-Ross 23


The Four Stages of Store

 

- Ifetch: Instruction Fetch
 - Fetch the instruction from the Instruction Memory
- Reg/Dec: Registers Fetch and Instruction Decode
- Exec: Calculate the memory address
- Mem: Write the data into the Data Memory

EEL-4713 Ann Gordon-Ross 24


The Four Stages of Beq

 

- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU compares the two register operands**
 - Adder calculates the branch target address
- **Mem: If the registers we compared in the Exec stage are the same,**
 - Write the branch target address into the PC

EEL-4713 Ann Gordon-Ross 25


A Pipelined Datapath

 

EEL-4713 Ann Gordon-Ross 26

The Instruction Fetch Stage

 
- Location 10: lw \$1, 0x100(\$2) \$1 ← Mem[(S2) + 0x100]



EEL-4713 Ann Gordon-Ross 27

A Detailed View of the Instruction Unit


- Location 10: lw \$1, 0x100(\$2)

 

EEL-4713 Ann Gordon-Ross 28

The Decode / Register Fetch Stage

 
° Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]



EEL-4713 Ann Gordon-Ross 29


Load's Address Calculation Stage

 ° Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]



EEL-4713 Ann Gordon-Ross 30


A Detailed View of the Execution Unit

 

EEL-4713 Ann Gordon-Ross 31

Load's Memory Access Stage

 
° Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]



EEL-4713 Ann Gordon-Ross 32

Load's Write Back Stage

 - Location 10: `lw $1, 0x100($2)` $\$1 \leftarrow \text{Mem}[(\$2) + 0x100]$




EEL-4713 Ann Gordon-Ross 33

How About Control Signals?

- Key Observation: Control Signals at Stage N = Func (Instr. at Stage N)
 - N = Exec, Mem, or Wr
 - IF and ID are the same for every instruction

 
- Example: Controls Signals at Exec Stage = Func(Load's Exec)



EEL-4713 Ann Gordon-Ross 34


Pipeline Control

 - The Main Control generates the control signals during Reg/Dec
 - Control signals for Exec (ExtOp, ALUSrc, ...) are used 1 cycle later
 - Control signals for Mem (MemWr Branch) are used 2 cycles later
 - Control signals for Wr (MemtoReg MemWr) are used 3 cycles later



EEL-4713 Ann Gordon-Ross 35

 Beginning of the Wr's Stage: A Real World Problem




- At the beginning of the Wr stage, we have a problem if:
 - RegAdr's (Rd or Rt) Clk-to-Q > RegWr's Clk-to-Q
- Similarly, at the beginning of the Mem stage, we have a problem if:
 - WrAdr's Clk-to-Q > MemWr's Clk-to-Q
- We have a race condition between Address and Write Enable!
 - Could write to incorrect address

EEL-4713 Ann Gordon-Ross 36

The Pipeline Problem

 
- Multiple Cycle design prevents race condition between Addr and WrEn:
 - Make sure Address is stable by the end of Cycle N
 - Asserts WrEn during Cycle N + 1
- This approach can NOT be used in the pipeline design because:
 - Must be able to write the register file every cycle
 - Must be able to write the data memory every cycle



EEL-4713 Ann Gordon-Ross 37


Synchronize Register File & Synchronize Memory

 - Solution: And the Write Enable signal with the Clock
 - Must consult circuit expert to ensure no timing violation:
 - Example: Clock High Time > Write Access Delay



EEL-4713 Ann Gordon-Ross 38

*A More Extensive Pipelining Example

 


- End of Cycle 4: Load's Mem, R-type's Exec, Store's Reg, Beq's Ifetch
- End of Cycle 5: Load's Wr, R-type's Mem, Store's Exec, Beq's Reg
- End of Cycle 6: R-type's Wr, Store's Mem, Beq's Exec
- End of Cycle 7: Store's Wr, Beq's Mem

EEL-4713 Ann Gordon-Ross 39


Pipelining Example: End of Cycle 4

 - 0: Load's Mem 4: R-type's Exec 8: Store's Reg 12: Beq's Ifetch



EEL-4713 Ann Gordon-Ross 40

The Delay Load Phenomenon

 

- Although Load is fetched during Cycle 1:
 - The data is NOT written into the Reg File until the end of Cycle 5
 - We cannot read this value from the Reg File until Cycle 6
 - 3-instruction delay before the load take effect
- This is referred to as Data Hazard:
 - Clever design techniques can reduce the delay to ONE instruction

Summary

- Disadvantages of the Single Cycle Processor
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- Multiple Clock Cycle Processor:
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- Pipeline Processor:
 - Natural enhancement of the multiple clock cycle processor
 - Each functional unit can only be used once per instruction
 - If a instruction is going to use a functional unit:
 - it must use it at the same stage as all other instructions
 - Pipeline Control:
 - Each stage's control signal depends ONLY on the instruction that is currently in that stage