

EEL-4713 Computer Architecture Multipliers and shifters

EEL-4713 Ann Gordon-Ross.1

Deriving requirements of ALU

- Start with instruction set architecture: must be able to do all operations in ISA
- Tradeoffs of cost and speed based on frequency of occurrence, hardware budget
- MIPS ISA

EEL-4713 Ann Gordon-Ross.3

Outline

- Multiplication and shift registers
 - Chapter 3, section 3.4
- Next lecture
 - Division, floating-point
 - 3.5 – 3.6

EEL-4713 Ann Gordon-Ross.2

MIPS arithmetic instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comments</i>
◦ add	add \$1,\$2,\$3	$S1 = S2 + S3$	3 operands; exception possible
◦ subtract	sub \$1,\$2,\$3	$S1 = S2 - S3$	3 operands; exception possible
◦ add immediate	addi \$1,\$2,100	$S1 = S2 + 100$	+ constant; exception possible
◦ add unsigned	addu \$1,\$2,\$3	$S1 = S2 + S3$	3 operands; no exceptions
◦ subtract unsigned	subu \$1,\$2,\$3	$S1 = S2 - S3$	3 operands; no exceptions
◦ add imm. unsigned	addiu \$1,\$2,100	$S1 = S2 + 100$	+ constant; no exceptions
◦ multiply	mult \$2,\$3	$Hi, Lo = S2 \times S3$	64-bit signed product
◦ multiply unsigned	multu \$2,\$3	$Hi, Lo = S2 \times S3$	64-bit unsigned product
◦ divide	div \$2,\$3	$Lo = S2 \div S3,$ $Hi = S2 \bmod S3$	Lo = quotient, Hi = remainder
◦ divide unsigned	divu \$2,\$3	$Lo = S2 \div S3,$ $Hi = S2 \bmod S3$	Unsigned quotient & remainder
◦ Move from Hi	mfhi \$1	$S1 = Hi$	Used to get copy of Hi
◦ Move from Lo	mflo \$1	$S1 = Lo$	Used to get copy of Lo

EEL-4713 Ann Gordon-Ross.4

MIPS ALU requirements

- Add, AddU, Sub, SubU, Addl, AddIU
=> 2's complement adder with overflow detection & inverter
- SLTI, SLTIU (set less than)
=> 2's complement adder with inverter, check sign bit of result
- BEQ, BNE (branch on equal or not equal)
=> 2's complement adder with inverter, check if result = 0
- And, Or, Andl, Orl
=> Logical AND, logical OR
- ALU from last lecture supports these ops

EEL-4713 Ann Gordon-Ross.5

MULTIPLY (unsigned)

- Paper and pencil example (unsigned):

```

Multiplicand      1000
Multiplier        1001
-----
1000
0000
0000
1000
-----
Product          01001000
    
```

- m bits x n bits = m+n bit product
- Binary makes it easy:
 - 0 => place 0 (0 x multiplicand)
 - 1 => place a copy (1 x multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement


EEL-4713 Ann Gordon-Ross.7

Additional MIPS ALU requirements

- Xor, Nor, Xorl
=> Logical XOR, logical NOR
- Sll, Srl, Sra
=> Need left shift, right shift, right shift arithmetic by 0 to 31 bits
- Mult, MultU, Div, DivU
=> Need 32-bit multiply and divide, signed and unsigned

EEL-4713 Ann Gordon-Ross.6


Unsigned Combinational Multiplier: A * B

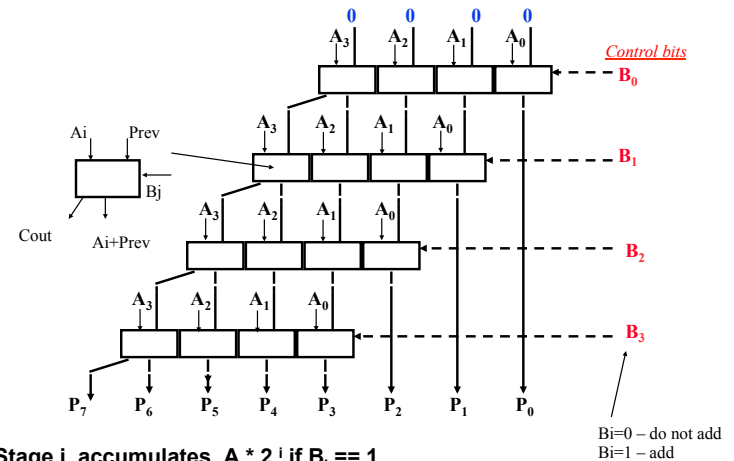

- Stage i accumulates $A * 2^i$ if $B_i == 1$
- Q: How much hardware for 32 bit multiplier? Critical path?

EEL-4713 Ann Gordon-Ross.8


How does it work?

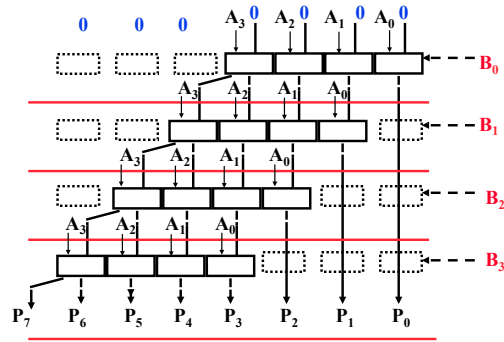

- at each stage, shift A left once more (effectively $A \times 2$)
- use next bit of B to determine whether to add in shifted multiplicand
- accumulate 2 n-bit partial products at each stage

EEL-4713 Ann Gordon-Ross.9

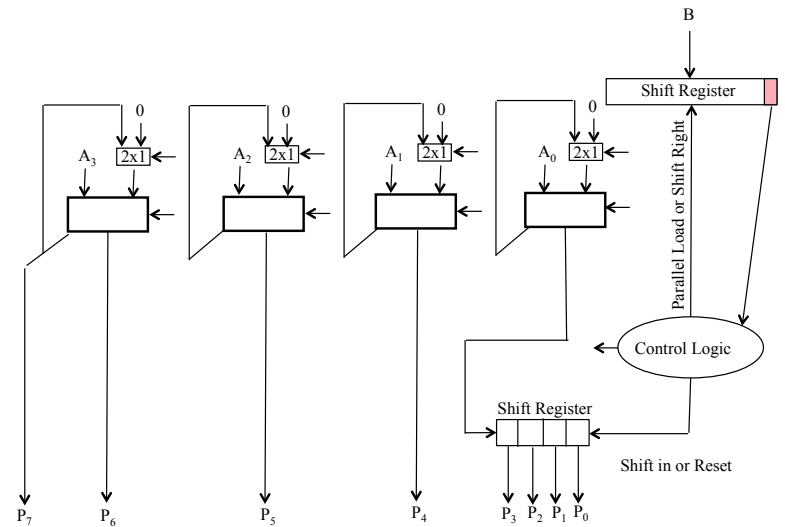Same principle, less hardware, multi-cycled



EEL-4713 Ann Gordon-Ross.10


Improvements

- Same operations in each step
 - Shift, add
 - Shift – hardwired; add: separate adders in each stage = LOTS OF HARDWARE!
- Can reduce size by performing one step per cycle, reusing the adder
 - Using a shift register rather than hard-wiring
 - Multi-cycle instead of one long cycle
- Advantage: uses less hardware, may be pipelined
- Disadvantage: it may be slower due to pipelining overhead and unbalanced pipeline stages

EEL-4713 Ann Gordon-Ross.11

Unsigned shift-add multiplier (version 1)

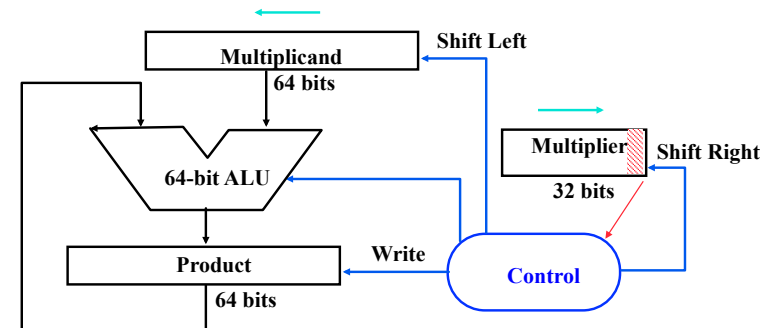
- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

EEL-4713 Ann Gordon-Ross.12

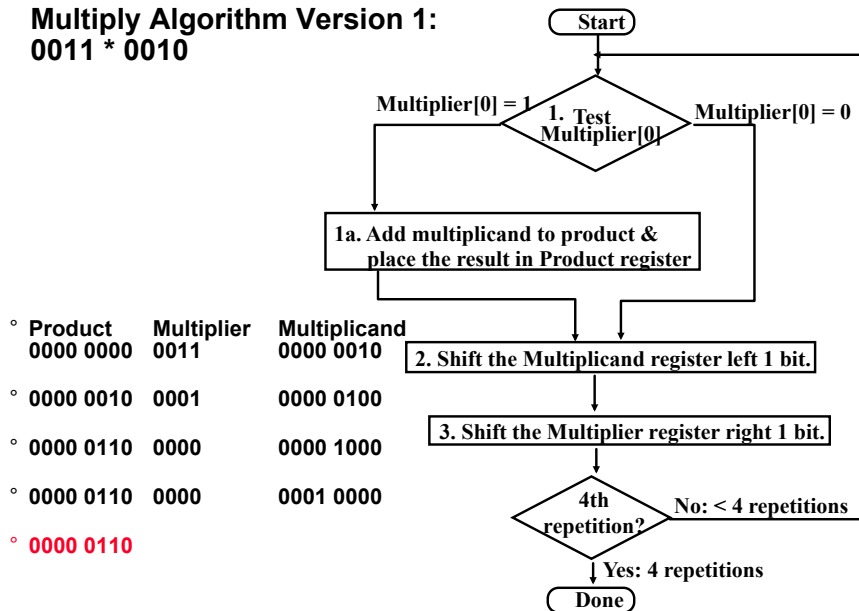Multiply Algorithm Version 1: 0011 * 0010



EEL-4713 Ann Gordon-Ross.13

Potential Optimizations

- In state 1:
 - Test multiplier for 0, exit
- Observation:
 - If multiplier[0] = 1, 2 cycles needed (add, then shifts)
 - If multiplier[0] = 0, 1 cycle needed (shifts only)
 - Before start, set multiplier and multiplicand intelligently
 - Multiplier as smallest value?
 - Find left-most 1 bit for each input, the right-most of those two bits is the smallest value, therefore exit sooner out of state 1
 - Multiplier as least number of ones?
 - X = 1000000 and Y = 0111111
 - If multiplier = X, 9 cycles
 - If multiplier = Y, 13 cycles

EEL-4713 Ann Gordon-Ross.14


Observations on Multiply Version 1

- 1 clock per add and shifts (can shift in parallel) => 32*2 clocks per multiply
- Half of bits in multiplicand always 0 => 64-bit adder is wasted
- 0's inserted in left of multiplicand as shifted => least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to right?

EEL-4713 Ann Gordon-Ross.15

MULTIPLY HARDWARE Version 2

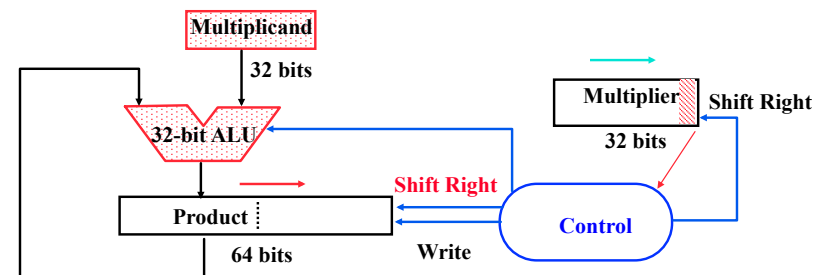
- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg



EEL-4713 Ann Gordon-Ross.16

*Multiply Algorithm Version 2

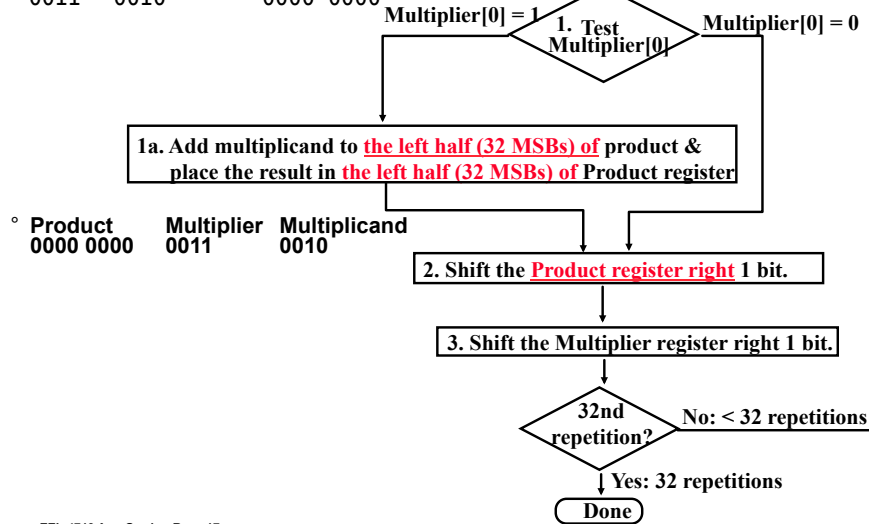
Multiplier Multiplicand Product
0011 0010 0000 0000



Product Multiplier Multiplicand
0000 0000 0011 0010

EEL-4713 Ann Gordon-Ross.17


What's going on?

 

◦ Multiplicand stays still and product moves right

EEL-4713 Ann Gordon-Ross.18

Multiply Algorithm Version 2

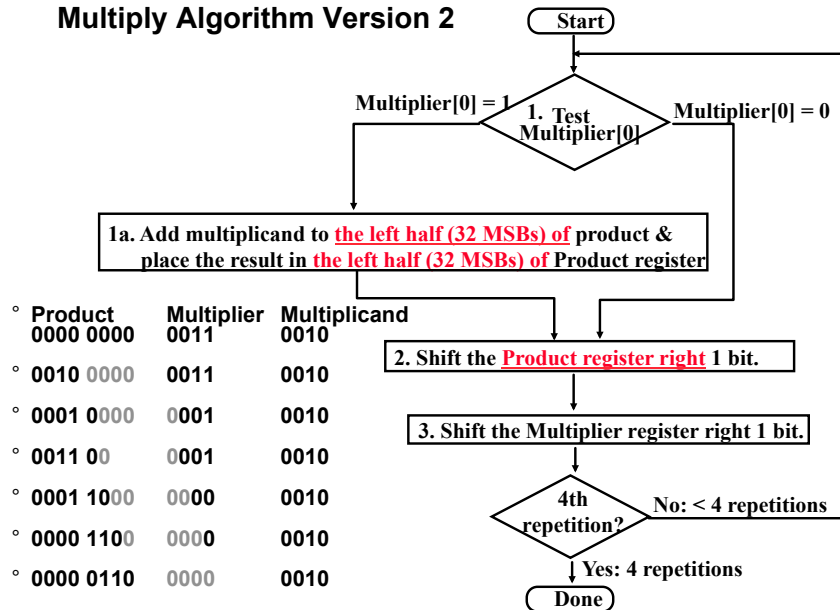


Product Multiplier Multiplicand
0000 0000 0011 0010
0010 0000 0011 0010
0001 0000 0001 0010
0011 00 0001 0010
0001 1000 0000 0010
0000 1100 0000 0010
0000 0110 0000 0010

EEL-4713 Ann Gordon-Ross.19

Observations on Multiply Version 2

 
◦ Wasted space in the product register exactly matches size of multiplier
=> combine Multiplier register and Product register



EEL-4713 Ann Gordon-Ross.20

MULTIPLY HARDWARE Version 3

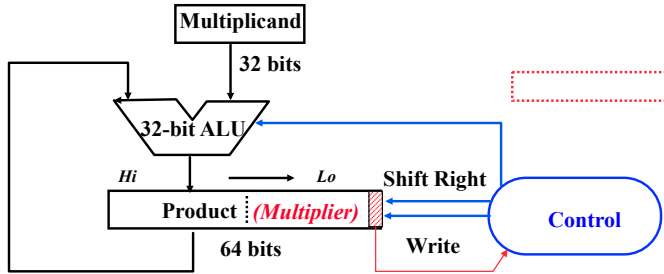
- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg, Multiplier stored in LSBs of Product)



EEL-4713 Ann Gordon-Ross.21

Multiply Algorithm Version 3

Multiplicand Product
0010 0000 0011

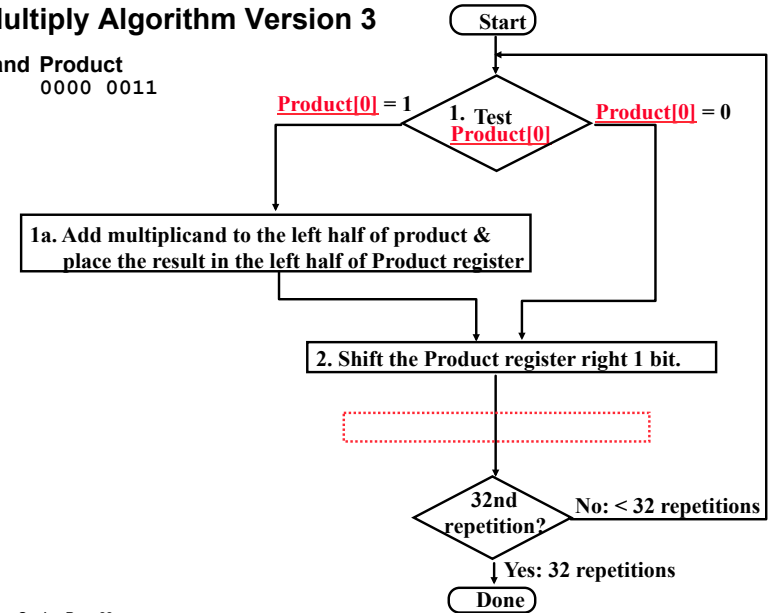

EEL-4713 Ann Gordon-Ross.22

Observations on Multiply Version 3

- MIPS registers Hi and Lo are left and right half of Product
- Gives us MIPS instruction MultU
- **How can you make it faster?**
- What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - apply definition of 2's complement
 - need to sign-extend partial products and subtract at the end
 - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
 - can handle multiple bits at a time

EEL-4713 Ann Gordon-Ross.23

Representing sequences of 1s as a difference

$$\begin{array}{cccccccc}
 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 \\
 & & & & 2^3 & 2^2 & 2^1 & 2^0 \\
 & & & & 8 + & 4 + & 2 + & 1 = 15 = 2^4 - 2^0 = 16 - 0
 \end{array}$$

$$\begin{array}{cccccccccccccccc}
 0 & 0 & 0 & 0 & \dots & 0 & 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 & 0 & 0 & 0 \\
 & & & & & & \swarrow & & & & & & & \searrow & & & \\
 & & & & & & 2^n + 2^{n-1} + \dots + 2^{n-8} & = & 2^{n+1} - 2^{n-8}
 \end{array}$$

EEL-4713 Ann Gordon-Ross.24

Representing sequences of 1s as a difference

- Why?
 - $x = 2^n + 2^{(n-1)} + \dots + 2^k$
 - $2x = 2^{(n+1)} + 2^n + \dots + 2^{(k+1)}$ (essentially shift left 1 bit)
 - $2x - x = [2^{(n+1)} + 2^n + \dots + 2^{(k+1)}] - [2^n + 2^{(n-1)} + \dots + 2^k]$
 - 2^n through $2^{(k+1)}$ cancel out
 - $x = 2^{(n+1)} - 2^k$

- How is this useful?
 - A sequence of (n-k) 1s in a multiplier
 - (n-k) adds, or
 - 1 add and 1 sub
 - Look at each sequence of 1s and add together

EEL-4713 Ann Gordon-Ross.25

Motivation for Booth's Algorithm


- Example $2 \times 6 = 0010 \times 0110$:

	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	00001100	

- Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one.

EEL-4713 Ann Gordon-Ross.26

Booth's Algorithm Insight

 

Current Bit	Bit to the Right	Explanation	Example
1	0	Beginning of a run of 1s	000111 <u>1</u> 000
1	1	Middle of a run of 1s	00011 <u>1</u> 1000
0	1	End of a run of 1s	000 <u>1</u> 111000
0	0	Middle of a run of 0s	<u>0</u> 01111000

Speed motivation if shift faster than add

Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one

EEL-4713 Ann Gordon-Ross.27


Booth's Algorithm

1. Depending on the current and previous bits, do one of the following:
 - 00: a. Middle of a string of 0s, so no arithmetic operations.
 - 01: b. End of a string of 1s, so add the multiplicand to the left half of the product.
 - 10: c. Beginning of a string of 1s, so subtract the multiplicand from the left half of the product.
 - 11: d. Middle of a string of 1s, so no arithmetic operation.
2. As in the previous algorithm, shift the Product register right (arith) 1 bit.

EEL-4713 Ann Gordon-Ross.28

Booth's Algorithm

Multiplicand Product
0010 0000 0011

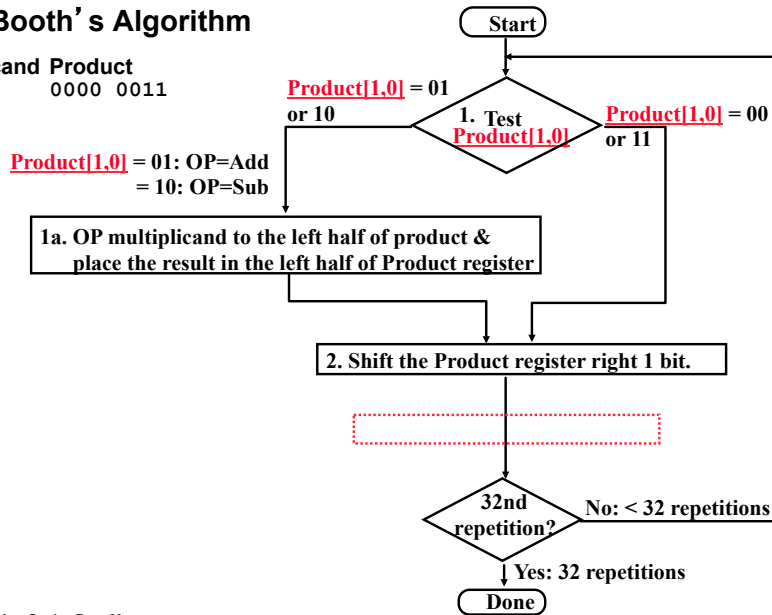

EEL-4713 Ann Gordon-Ross.29

Booths Example: 2 (0010) * 7 (0111) = 14 (0000 1110)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 0111 0	10 -> sub
1a. P = P - m	1110	1110 0111 0	shift P (sign ext)
1b.	0010	1111 0011 1	11 -> nop, shift
2.	0010	1111 1001 1	11 -> nop, shift
3.	0010	1111 1100 1	01 -> add
4a.	0010	0001 1100 1	shift
4b.	0010	0000 1110 0	done
		14	

EEL-4713 Ann Gordon-Ross.30

Booths Example: 2 (0010) * -3 (1101) = -6 (1111 1010)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 1101 0	10 -> sub
1a. P = P - m	1110	1110 1101 0	shift P (sign ext)
1b.	0010	1111 0110 1	01 -> add
2a.		0001 0110 1	shift P
2b.	0010	0000 1011 0	10 -> sub
3a.	0010	1110 1011 0	shift
3b.	0010	1111 0101 1	11 -> nop
4a.		1111 0101 1	shift
4b.	0010	1111 1010 1	done

Neg. 6

EEL-4713 Ann Gordon-Ross.31

MIPS logical instructions

Instruction	Example	Meaning	Comment
and	and \$1,\$2,\$3	\$1 = \$2 & \$3	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	\$1 = \$2 \$3	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	\$1 = \$2 ⊕ \$3	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	\$1 = ~(\$2 \$3)	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	\$1 = \$2 & 10	Logical AND reg, constant
or immediate	ori \$1,\$2,10	\$1 = \$2 10	Logical OR reg, constant
xor immediate	xori \$1,\$2,10	\$1 = \$2 & ~10	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	\$1 = \$2 << 10	Shift left by constant
shift right logical	srl \$1,\$2,10	\$1 = \$2 >> 10	Shift right by constant
shift right arithm.	sra \$1,\$2,10	\$1 = \$2 >> 10	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	\$1 = \$2 << \$3	Shift left by variable
shift right logical	srlv \$1,\$2,\$3	\$1 = \$2 >> \$3	Shift right by variable
shift right arithm.	srav \$1,\$2,\$3	\$1 = \$2 >> \$3	Shift right arith. by variable (sign extend)

EEL-4713 Ann Gordon-Ross.32


Shifters

Three different kinds:

logical-- value shifted in is always "0"



 arithmetic-- on right shifts, sign extend




rotating-- shifted out bits are wrapped around (not in MIPS)




Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Combinational Shifter from MUXes

 

◦ How many levels for 32-bit shifter?

 General Shift Right Scheme using 16 bit example



If added Right-to-left connections could support Rotate (not in MIPS but found in other ISAs)

Summary

- Instruction Set drives the ALU design
- Multiply: successive refinement to see final design
 - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
 - Booth's algorithm to handle signed multiplies
- What's Missing from MIPS is Divide & Floating Point Arithmetic